

Semester: **Spring 2024**
Course Code: **CSE460**
Course Title: **VLSI Design**


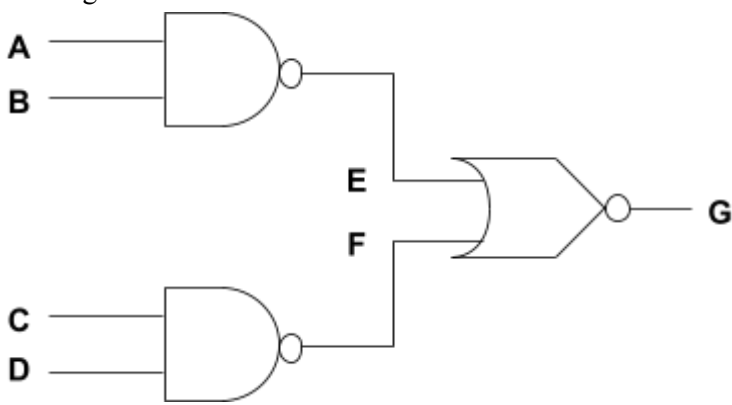
Final Exam
Full Marks: **15 x 3 = 45**
Time: **1 hour 30 minutes**
Date: **7th May, 2024**

Set A

Student ID:	Name:	Section:
-------------	-------	----------

[Answer all questions. Each question carries equal marks.]

[After the exam, the question paper should be turned in along with the answer script.]

1. (CO3)	(i)	Consider the following logic function: $Y = (A+B) \cdot (C+D) \cdot (E.F)$	
		(a) Draw the stick diagram.	7
		(b) Estimate the total layout area.	3
	(ii)	(a) Briefly explain why Lithography is used in CMOS fabrication.	3
		(b) Draw the required masks to fabricate the following. 	2
2. (CO1)	Consider the following circuit:  <p>The switching probabilities of nodes A, B, C, D and basic logic gates along with the node capacitances of E, F, G are given below:</p>		

Node	Switching probability
A	0.4
B	0.7
C	0.8
D	0.5

Gate	Switching probability
AND	$P_1 P_2$
OR	$1 - (1 - P_1)(1 - P_2)$
NOT	$1 - P$

Node	Capacitance (nF)
E	4
F	6
G	5

Explanation of the second table: Say, an AND gate has two input nodes with switching probabilities of P_1 and P_2 . The switching probability of the output node will be $P_1 * P_2$.


Now, if P_i is the switching probability of any node i , the activity factor of that node can be calculated using the following equation:

$$\alpha_i = P_i(1 - P_i)$$


For the nodes **E**, **F** and **G**:

(a)	Calculate the switching probabilities.	6
(b)	Determine the activity factors.	3
(c)	Calculate the switching power losses.	6

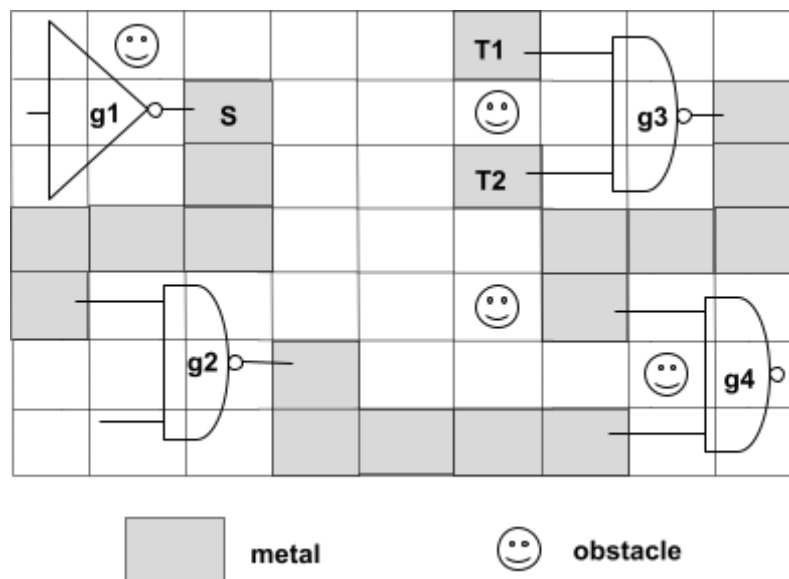
3. (CO4) In the following figure, you can see the grids for Lee's Maze Algorithm.




(a)	Using the algorithm, find the <u>shortest</u> path from S to T1 and T2 allowing minimum bends. Answer this question on the next page of the question paper.	6
(b)	Show the graph representation of the connected gates ignoring the grids. (Convert gates to nodes).	3
(c)	Compare the initial cut cost with that of after the first iteration of the KL algorithm for partitioning. Assume initial Cut Sets: A (g1,g2) and B (g3,g4).	6

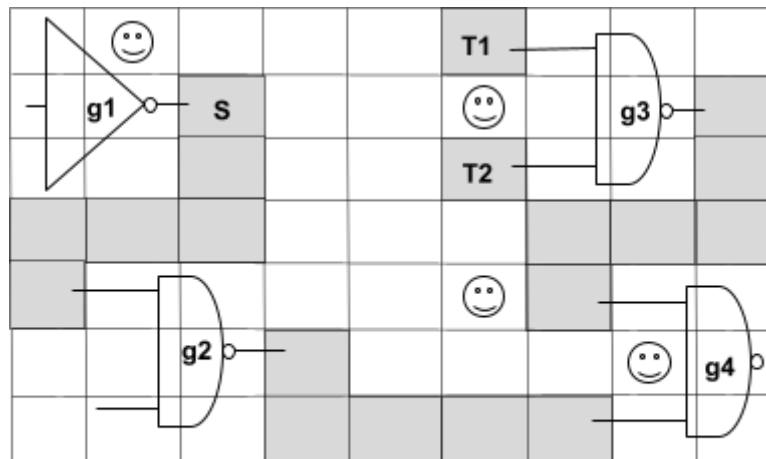

 metal  obstacle

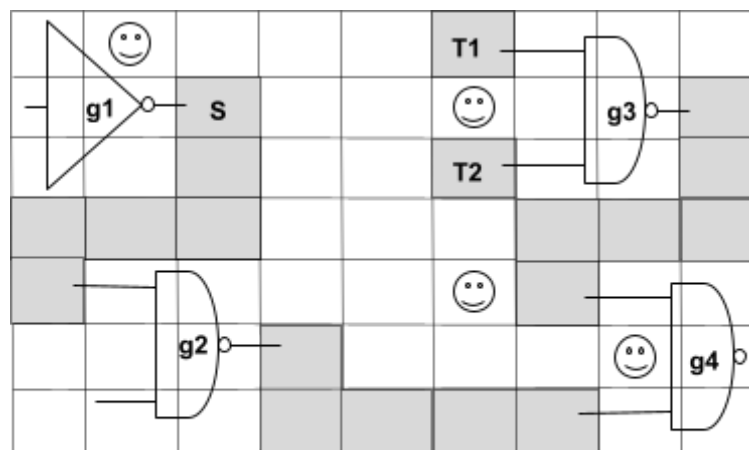

 metal  obstacle

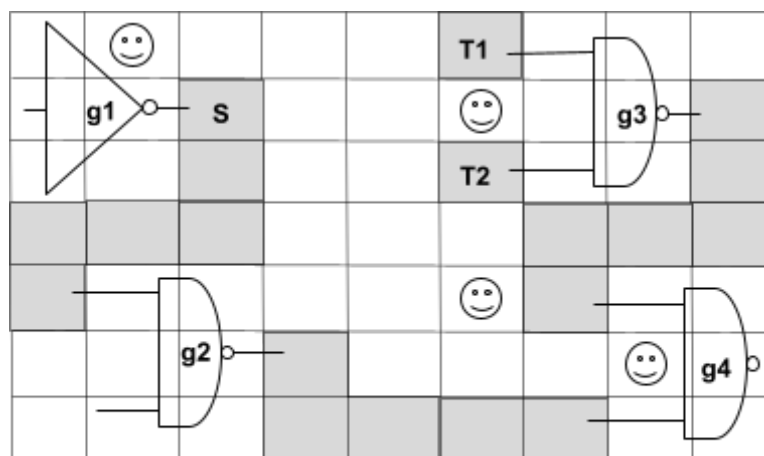

 metal  obstacle