

CSE 460: VLSI Design

Lecture 9: Finite State Machines (part 2)

Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)


| | | | | | | | | | | | |
|--------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

Figure 6.22 Sequences of input and output signals.

Steps->

- State diagram
- State table
- State assigned table
- K-map
- Circuit

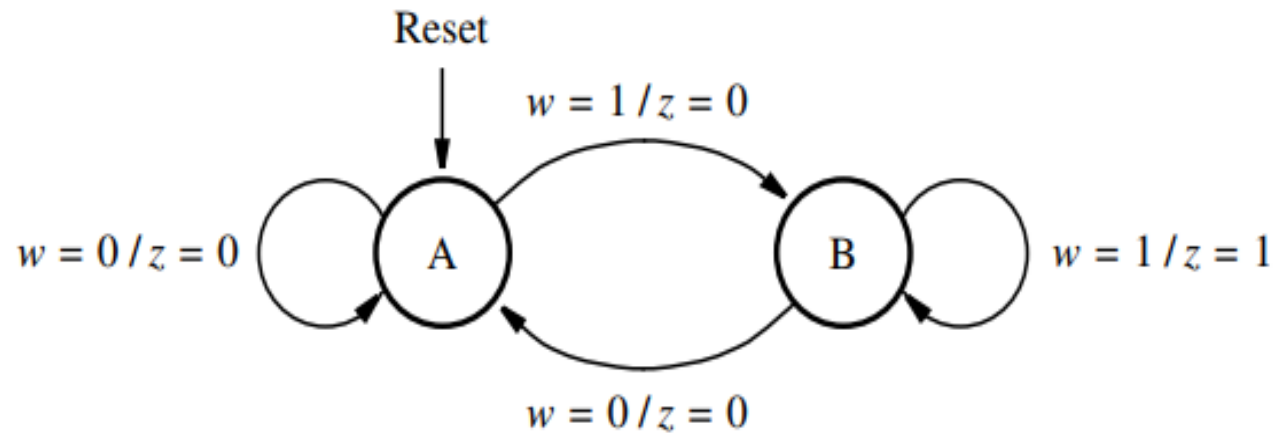Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)



Steps->

- **State diagram**
- State table
- State assigned table
- K-map
- Circuit

Figure 6.23 State diagram of an FSM that realizes the task in Figure 6.22.

Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)

| Present state | Next state | | Output z | |
|---------------|------------|---------|------------|---------|
| | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| A | A | B | 0 | 0 |
| B | A | B | 0 | 1 |

Figure 6.24 State table for the FSM in Figure 6.23.

Steps->

- State diagram
- **State table**
- **State assigned table**
- K-map
- Circuit

| | Present state | Next state | | Output | |
|---|---------------|------------|---------|---------|---------|
| | | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| | y | Y | Y | z | z |
| A | 0 | 0 | 1 | 0 | 0 |
| B | 1 | 0 | 1 | 0 | 1 |

Figure 6.25 State-assigned table for the FSM in Figure 6.24.

Note that,

➤ $Y = f(w, y)$

➤ $z = f(w, y)$

Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)

Y =>

| y \ w | 0 | 1 |
|-------|---|---|
| 0 | 0 | 1 |
| 1 | 0 | 1 |

$$Y = w$$

z =>

| y \ w | 0 | 1 |
|-------|---|---|
| 0 | 0 | 0 |
| 1 | 0 | 1 |

$$z = wy$$


Steps->

- State diagram
- State table
- State assigned table
- **K-map** (Y and z)
- Circuit

Note that,

- $Y = f(w, y)$
- $z = f(w, y)$

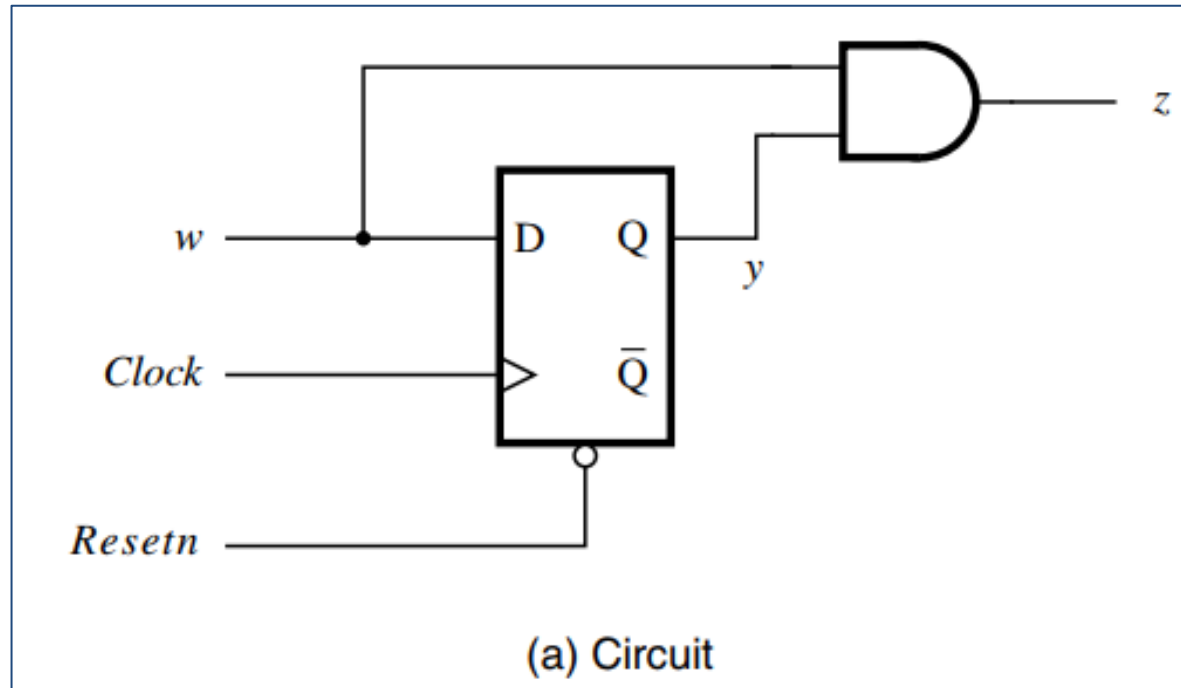Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)



Steps->

- State diagram
- State table
- State assigned table
- K-map
- **Circuit**

Encoding Schemes (State Assignment)

Consider a state assigned table below:

| | Present state | Next state | | Output z |
|----------|------------------|------------|-----------|-------------------|
| | | $w=0$ | $w=1$ | |
| | $y_2 y_1$ | $Y_2 Y_1$ | $Y_2 Y_1$ | |
| A | 00 | 00 | 01 | 0 |
| B | 01 | 00 | 10 | 0 |
| C | 10 | 00 | 10 | 1 |
| | 11 | dd | dd | d |

Schemes->

- **Binary encoding**
- Gray encoding
- One-hot encoding

Encoding Schemes (State Assignment)

Consider another state assigned table below:

| | Present state | Next state | | Output z |
|----------|------------------|------------|-----------|-------------------|
| | | $w=0$ | $w=1$ | |
| | $y_2 y_1$ | $Y_2 Y_1$ | $Y_2 Y_1$ | |
| A | 00 | 00 | 01 | 0 |
| B | 01 | 00 | 11 | 0 |
| C | 11 | 00 | 11 | 1 |
| | 10 | dd | dd | d |

Schemes->

- Binary encoding
- **Gray encoding**
- One-hot encoding

| Decimal Number | 4 bit Binary Number | 4 bit Gray Code |
|----------------|------------------------|---|
| | <u>ABCD</u> | <u>G₁G₂G₃G₄</u> |
| 0 | 0 0 0 0 | 0 0 0 0 |
| 1 | 0 0 0 1 | 0 0 0 1 |
| 2 | 0 0 1 0 | 0 0 1 1 |
| 3 | 0 0 1 1 | 0 0 1 0 |
| 4 | 0 1 0 0 | 0 1 1 0 |
| 5 | 0 1 0 1 | 0 1 1 1 |
| 6 | 0 1 1 0 | 0 1 0 1 |
| 7 | 0 1 1 1 | 0 1 0 0 |
| 8 | 1 0 0 0 | 1 1 0 0 |
| 9 | 1 0 0 1 | 1 1 0 1 |
| 10 | 1 0 1 0 | 1 1 1 1 |
| 11 | 1 0 1 1 | 1 1 1 0 |
| 12 | 1 1 0 0 | 1 0 1 0 |
| 13 | 1 1 0 1 | 1 0 1 1 |
| 14 | 1 1 1 0 | 1 0 0 1 |
| 15 | 1 1 1 1 | 1 0 0 0 |

Encoding Schemes (State Assignment)

Consider another state assigned table below:

| | Present state $y_3y_2y_1$ | Next state | | Output z |
|---|---------------------------------|-------------|-------------|---------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_3Y_2Y_1$ | $Y_3Y_2Y_1$ | |
| A | 0 0 1 | 0 0 1 | 0 1 0 | 0 |
| B | 0 1 0 | 0 0 1 | 1 0 0 | 0 |
| C | 1 0 0 | 0 0 1 | 1 0 0 | 1 |

Schemes->

- Binary encoding
- Gray encoding
- **One-hot encoding**

How many flipflops are required? **Ans: 3**