

Semester: **Summer 2022**
Course Code: **CSE460**
Course Title: **VLSI Design**


Midterm Exam
Full Marks: **15 x 3 = 45**
Time: **1 hour 30 minutes**
Date: **9th September 2022**

Set B

Student ID:	Name:	Section:
-------------	-------	----------

[Answer any **THREE** questions out of **FOUR**. Each question carries equal marks.]

[After the exam, the question paper should be turned in along with the answer script.]

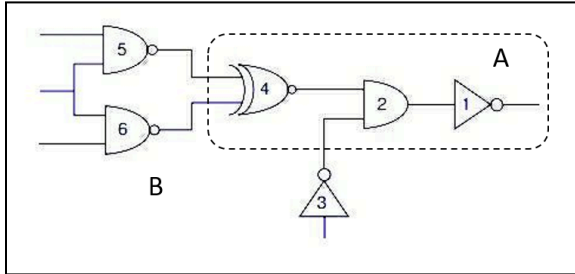1. (CO4, CO5)	<p>Mr. Roosevelt is a VLSI engineer in a renowned chip manufacturing company. He sets the physical positions of all the components on a chip to optimize the delay and power consumption. Suppose, Mr. Roosevelt is working on a chip that consists of 6 nodes illustrated in the figure below. Firstly, he partitions the nodes into two equal-sized blocks, and then, using the Kernighan-Lin algorithm, he minimizes the number of connections between the blocks. After floor-planning, placement, and maintaining all other design considerations, Mr. Roosevelt can dispatch the chip to the fabrication unit.</p>  <p>The dotted line in the figure represents the initial partitioning with A (1,2,4) & B (3,5,6) blocks. <u>For the first iteration</u>, answer the following:</p>	
	(a) Draw the corresponding graph representation of the above circuit.	2
	(b) Find the initial cut cost.	2
	(c) Calculate the cost of each node.	3
	(d) Evaluate necessary gains (Δg) for the first iteration.	4
	(e) Perform the first swap and compare the new cut cost with the initial one.	4

2. (CO3)	Consider a CMOS inverter in a 45 nm 1 V process, where the pMOS transistor has 4 times the width of the nMOS transistor. The ratio of electron mobility to hole mobility is 3:2 , and the threshold voltages are $ V_{tp} = V_{tn} = 0.15 \text{ V}$. Assume all other parameters are the same for both of the transistors.					
	(a)	Calculate the beta ratio (r) of the inverter.				3
	(b)	Determine the inverter threshold voltage (V_{inv}).				3
	(c)	Draw an approximate transfer characteristic curve (V_{out} vs V_{in}) for the inverter.				3
	(d)	Plot the I_{ds} vs. V_{ds} curve for the nMOS using the following values of V_{ds} . Given, $V_{gs} = 0.4 \text{ V}$, and $\beta_n = 140 \mu\text{A/V}^2$. Evaluate $V_{ds(sat)}$ and show the value of $V_{ds(sat)}$ in the plot. [6]				6
	V_{ds}		0.10 V	0.15 V	0.20 V	
3. (CO3)	A CMOS compound gate, $Y = \overline{A + B + C}$ is driving h identical CMOS compound gates with same function in a 1 μm process					
	(a)	Identify and design the CMOS circuit (indicate both nMOS and pMOS networks).				2
	(b)	Determine the individual transistor widths k_{nMOS} and k_{pMOS} to achieve the effective rise and fall resistance equal to that of a unit inverter, R , in the worst case.				2
	(c)	Sketch the simplified RC circuit.				5
	(d)	Derive the expressions for t_{pdf} and t_{cdf} . (Sketch the corresponding RC network from part (c) to derive the expressions.)				6
4. (CO3, CO4)	(a)	Consider the following logic circuit, which is being driven by a system frequency of 1 GHz and a supply voltage of 3.2 V . The inputs to the circuit are A, B, C , and D , while the output node is Y . N₁ and N₂ are two intermediate nodes. The activity factors of nodes N₁ , N₂ , and Y with respect to the system frequency are given in table 1. The input and output capacitances of the individual logic gates are listed in table 2.				
[continued to the next page]						

 


Figure: Logic circuit for problem 4 (a) (i), 4 (a) (ii)

Table 1

Node	Activity factor
N ₁	$\frac{1}{4}$
N ₂	$\frac{1}{4}$
Y	$\frac{15}{16}$

Table 2

Gate	Input capacitance	Output capacitance
NAND-2	4 pF	6 pF
NOR-2	5 pF	6 pF

- 1 GHz = 10^9 Hz
- 1 pF = 10^{-12} F

(i)	Find out the total capacitances at nodes N ₁ , N ₂ , and Y.	3
(ii)	Compute the total switching power of the logic circuit, assuming no power is being consumed at nodes A, B, C, and D.	8
(b)	Prove that a pMOS transistor cannot properly pass a low voltage signal (corresponding to a logical 0).	4