










## **Lecture 4: CMOS Implementation of logic blocks and sequential elements**

# Signal Strength

- ❑ *Strength* of signal
  - How close it approximates ideal voltage source
- ❑  $V_{DD}$  and GND rails are strongest 1 and 0
- ❑ nMOS pass strong 0
  - But degraded or weak 1
- ❑ pMOS pass strong 1
  - But degraded or weak 0
- ❑ Thus **nMOS are best for pull-down network**
- ❑ And, **pMOS are best for pull-up network**


# Pass Transistors

- Transistors can be used as switches

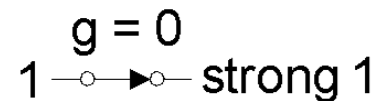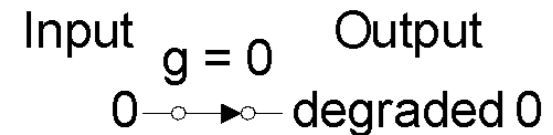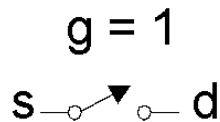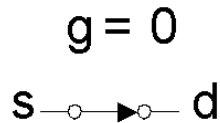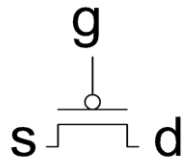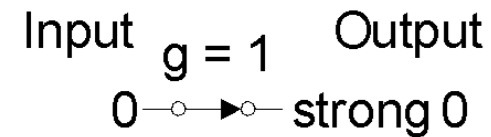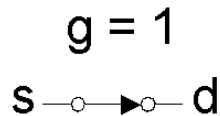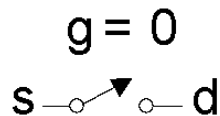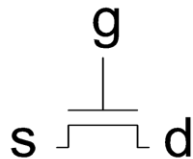

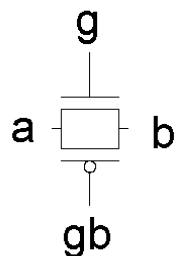
# Transmission Gates


- ❑ Pass transistors produce degraded outputs
- ❑ *Transmission gates* pass both 0 and 1 well



$g = 0, gb = 1$

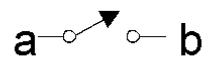

$g = 1, gb = 0$

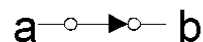

Input




Output

$g = 1, gb = 0$

0 → strong 0

$g = 1, gb = 0$



1 → strong 1

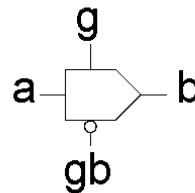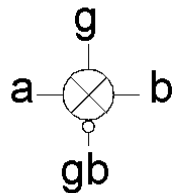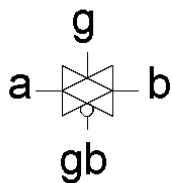

# Tristates


- ❑ *Tristate buffer* produces Z when not enabled

EN	A	Y
0	0	
0	1	
1	0	
1	1	

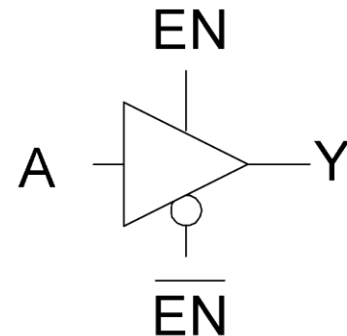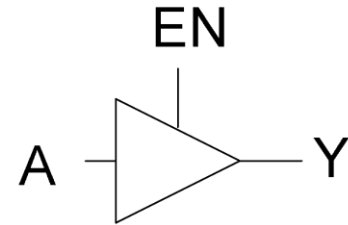

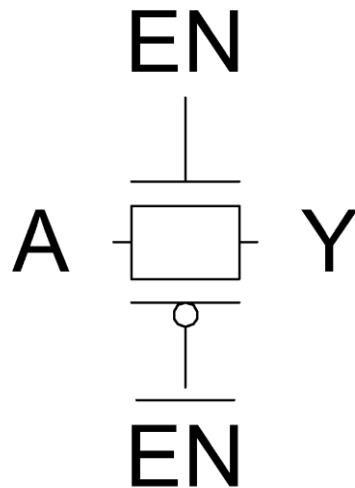
# Nonrestoring Tristate

- ❑ Transmission gate acts as tristate buffer
  - Only two transistors
  - But *nonrestoring*
    - Noise on A is passed on to Y


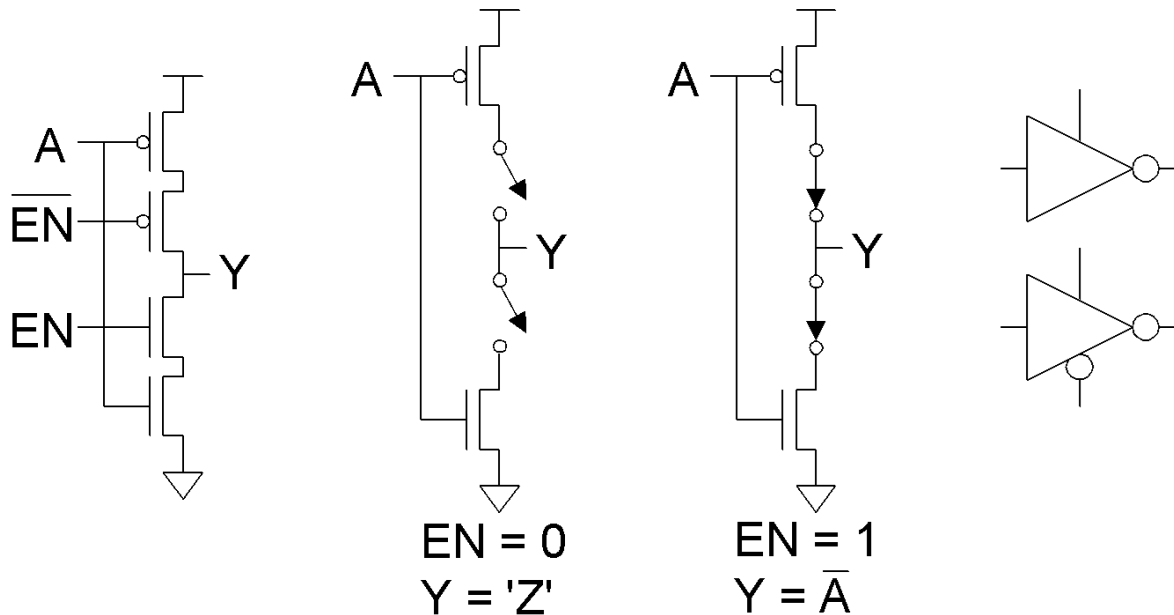
# Tristate Inverter


- ❑ Tristate inverter produces restored output
  - Violates conduction complement rule
  - Because we want a Z output



# Multiplexers

- ❑ 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	
0	X	1	
1	0	X	
1	1	X	

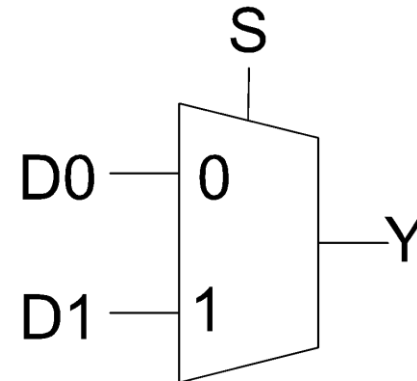




# Gate-Level Mux Design

- ❑  $Y = SD_1 + \bar{S}D_0$  (too many transistors)
- ❑ How many transistors are needed?



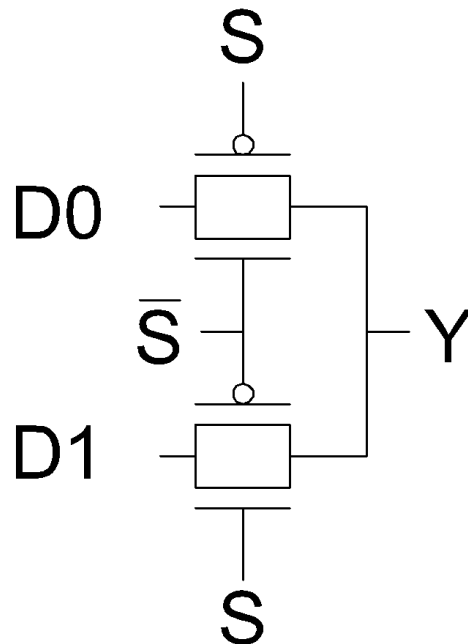
# Transmission Gate Mux

- ❑ Nonrestoring mux uses two transmission gates
  - Only 4 transistors



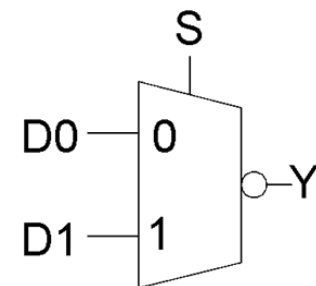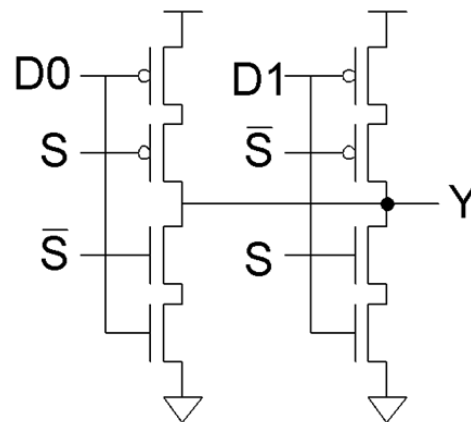
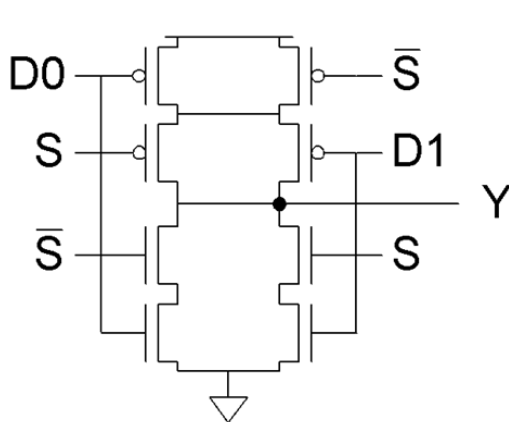
# Inverting Mux

- ❑ Inverting multiplexer
  - Use compound AOI22
  - Or pair of tristate inverters
  - Essentially the same thing
- ❑ Noninverting multiplexer adds an inverter



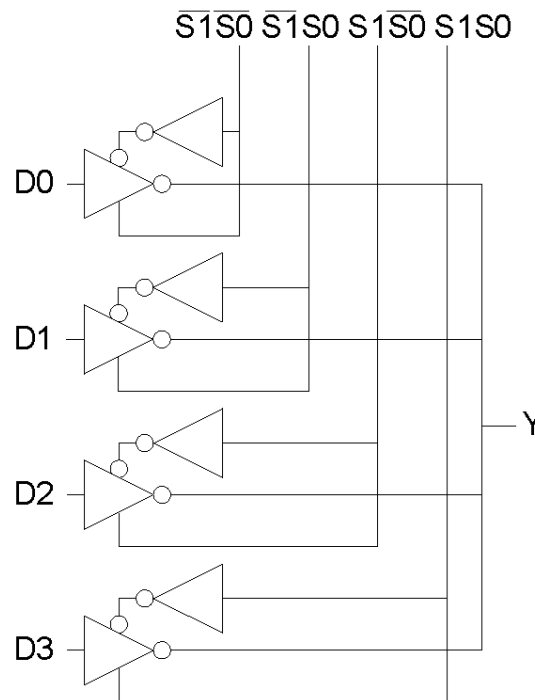
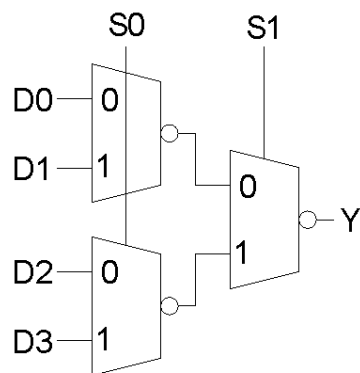
# 4:1 Multiplexer

- ❑ 4:1 mux chooses one of 4 inputs using two selects
  - Two levels of 2:1 muxes
  - Or four tristates



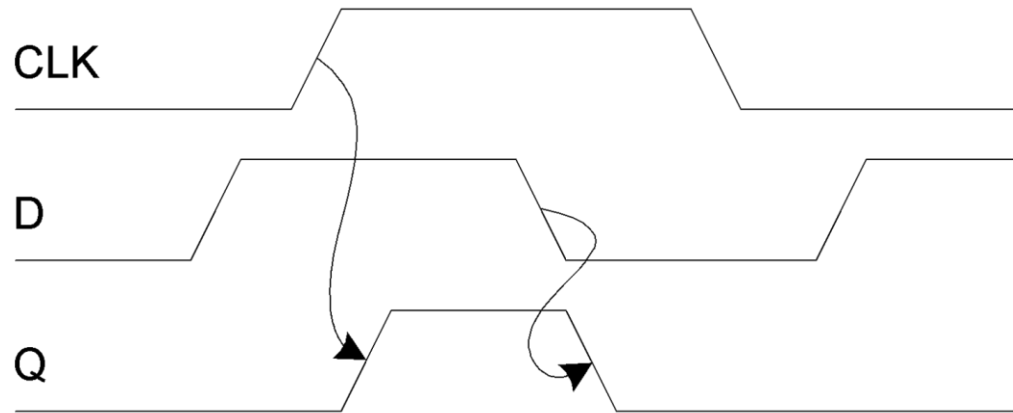
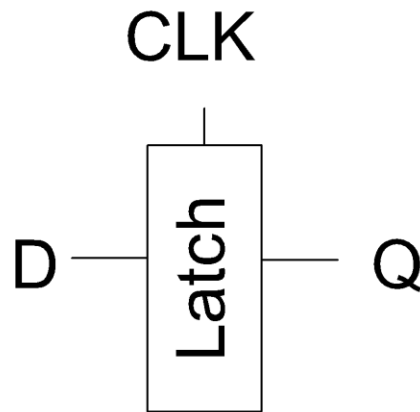
# D Latch

- ❑ When  $CLK = 1$ , latch is *transparent*
  - D flows through to Q like a buffer
- ❑ When  $CLK = 0$ , the latch is *opaque*
  - Q holds its old value independent of D
- ❑ a.k.a. *transparent latch* or *level-sensitive latch*






# D Latch Design

- ❑ Multiplexer chooses D or old Q

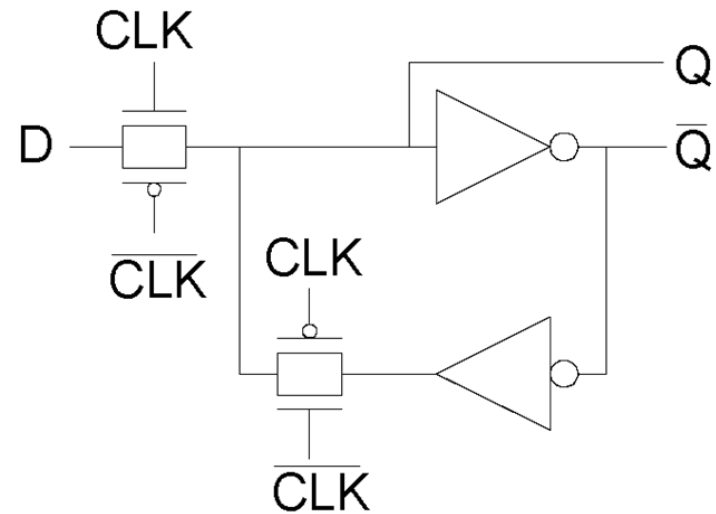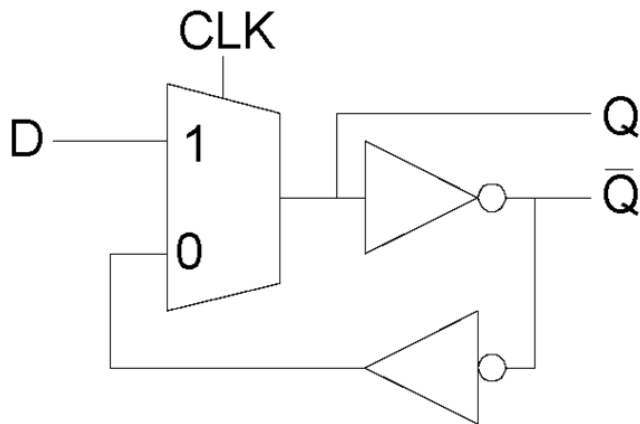


# D Latch Operation

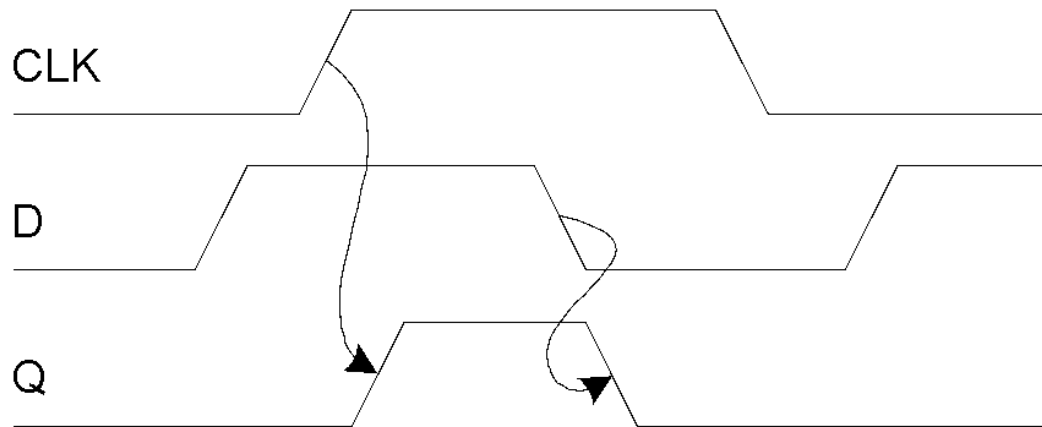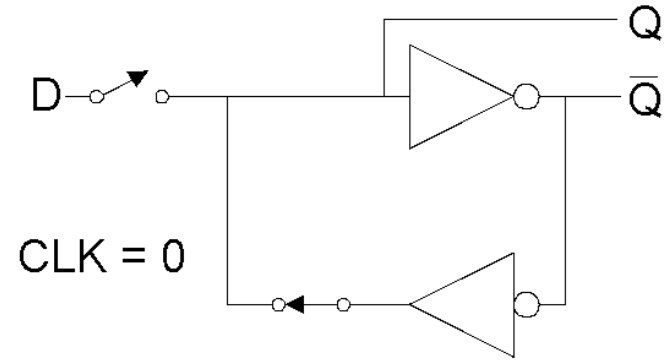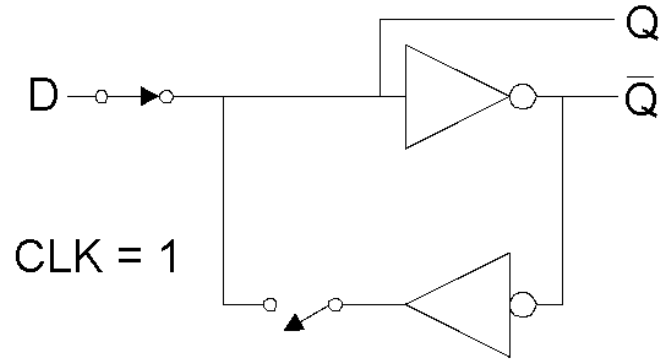
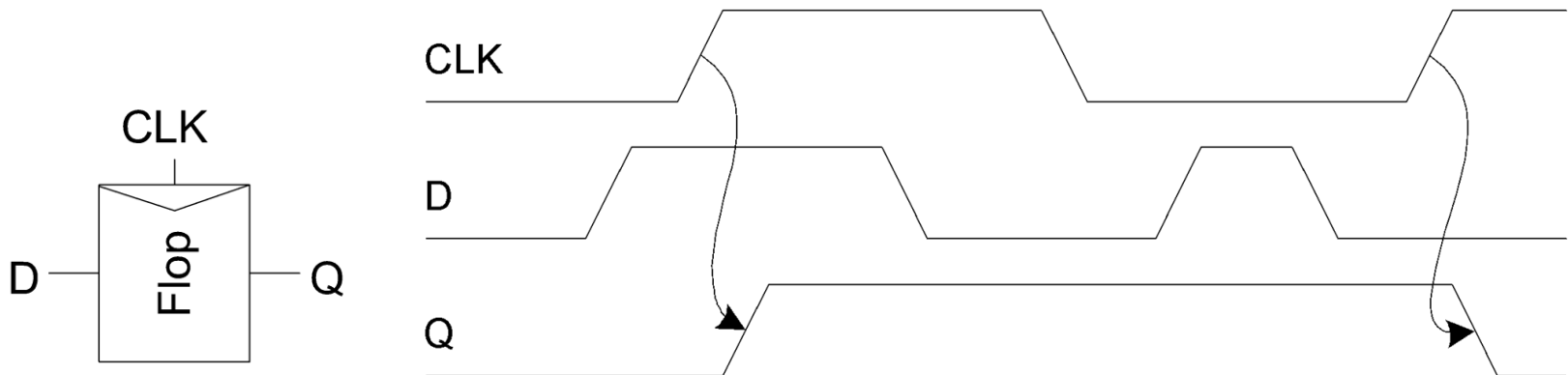
# D Flip-flop


- ❑ When CLK rises, D is copied to Q
- ❑ At all other times, Q holds its value
- ❑ a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*





# D Flip-flop Design

- Built from master and slave D latches

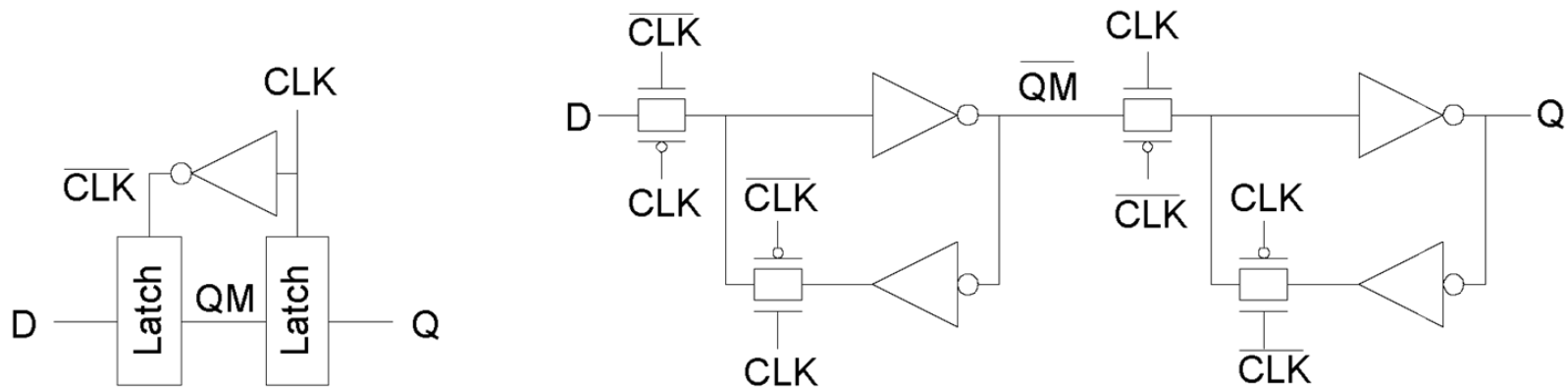

# D Flip-flop Operation

