

BRAC UNIVERSITY
CSE460
VLSI DESIGN
Assignment - 1

Name:

ID:

Section:


Question 1:[10 Marks]

Design a CMOS implementation of the following functions:

(a) $Y = ((A \cdot B \cdot C) + D) \cdot E$

(b) $Y = (A + (B \cdot C)) \cdot (D + E)$

(a)

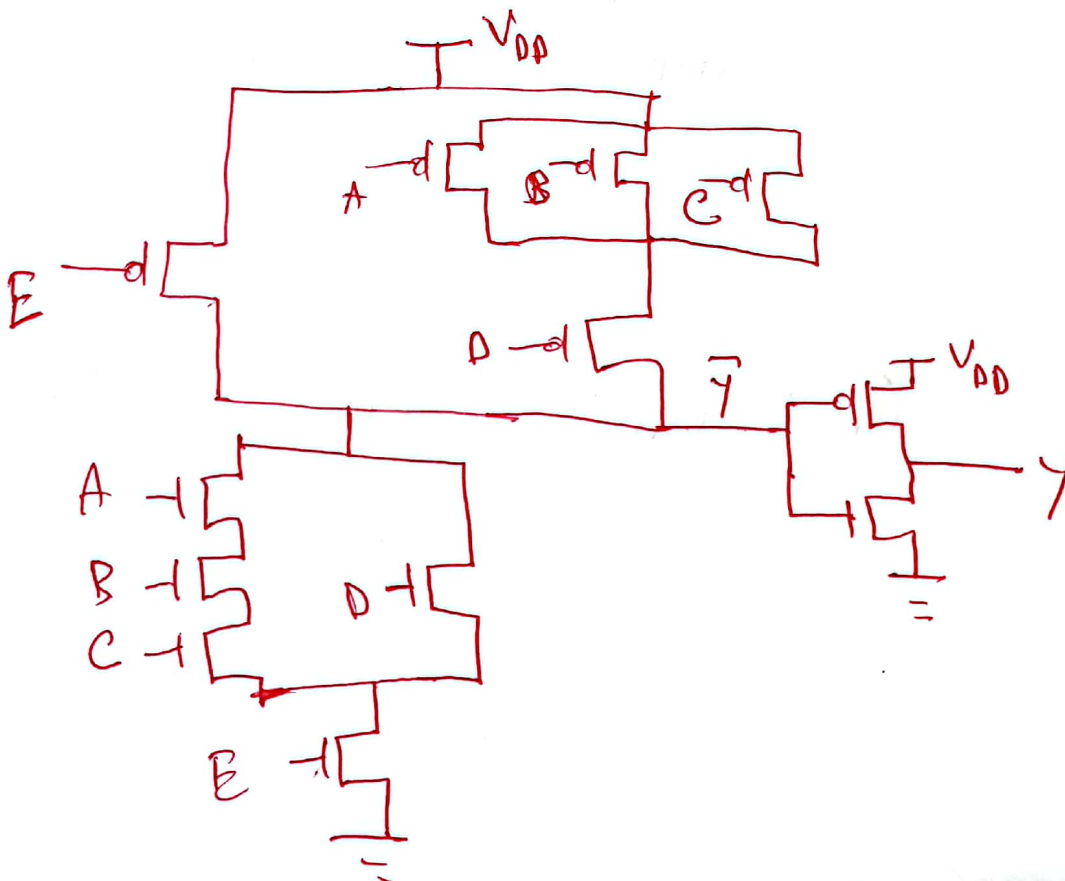

BRAC UNIVERSITY
CSE460
VLSI DESIGN
Assignment - 1

Name:

ID:

Section:


Question 1:[10 Marks]

Design a CMOS implementation of the following functions:


(a) $Y = ((A \cdot B \cdot C) + D) \cdot E$

(b) $Y = (A + (B \cdot C)) \cdot (D + E)$

(b)

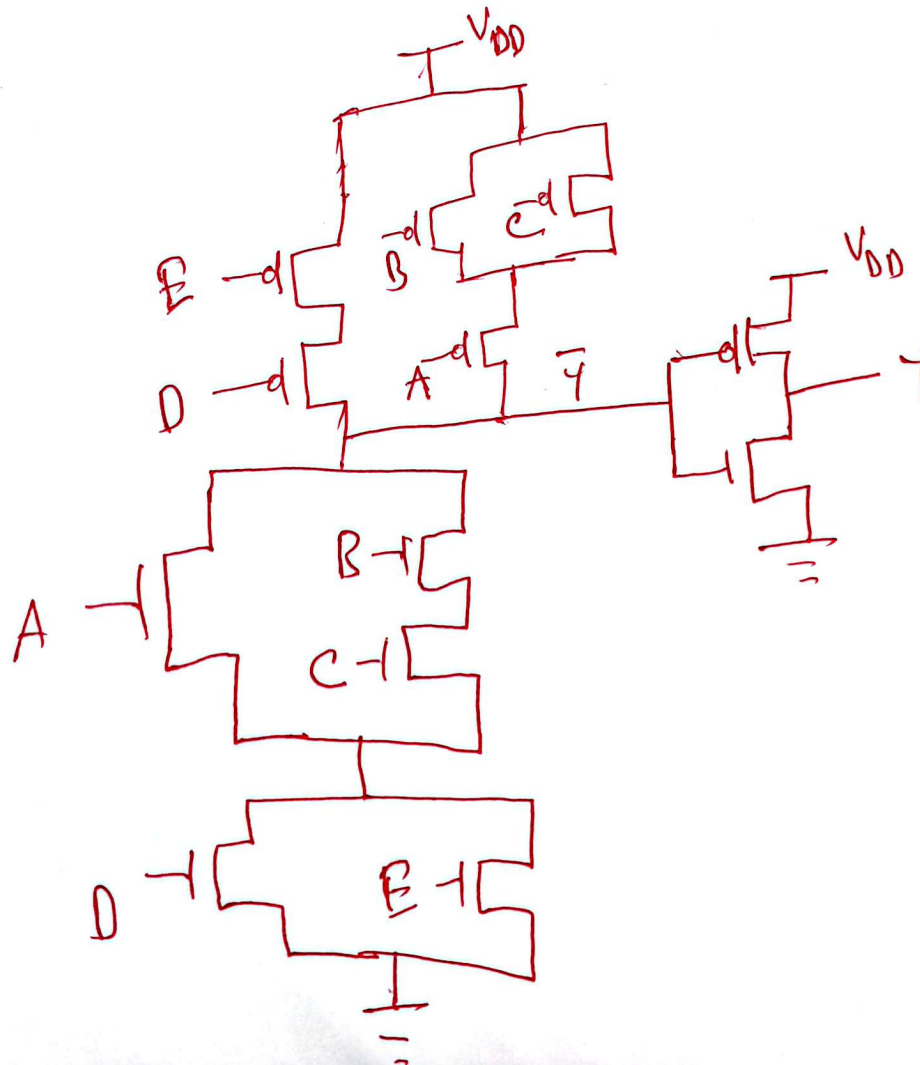


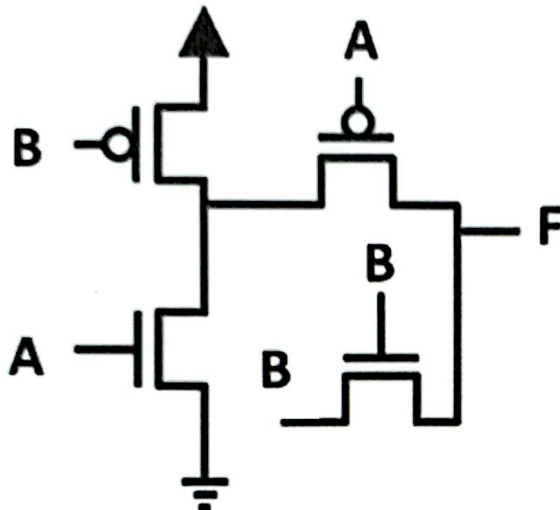Complete the truth table from the given circuit. Floating state or Z is also a possible answer.




A	B	F
0	0	1
0	1	1
1	0	0
1	1	1


Question 3:[10 Marks]

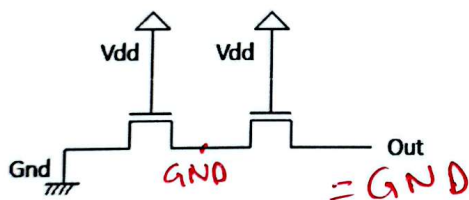


(a)

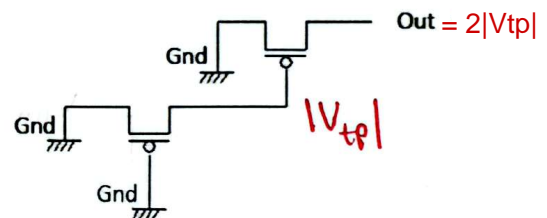

(b)

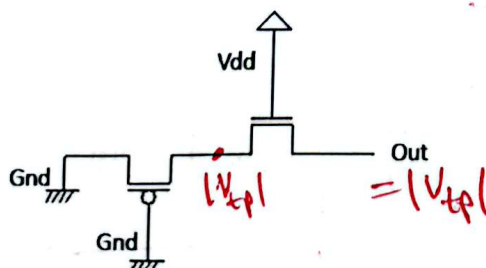

(c)

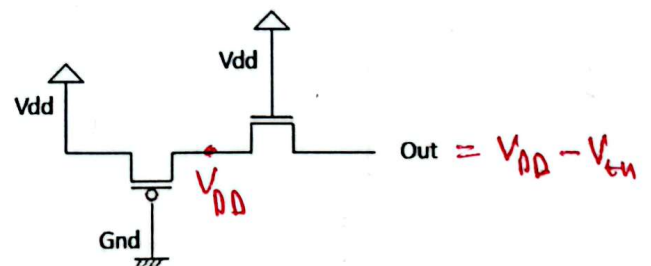

(d)

Find the value of Out for each of the above pass transistor circuits.

Question 4: [20 Marks]

Consider you need to design a temperature control system for your classroom at BRAC University. Your system has 1 Output **D**, and 3 inputs **A**, **B**, and **C** that come directly from three different sensors installed in the room. When a certain threshold of the temperature is crossed, each sensor gives a logical **HIGH** output. Your logic circuit should turn on the AC (**D = 1**) when the **majority** of inputs are **HIGH**.

- (a) Convert the problem statement into a Truth Table and write the simplified Boolean expression.
- (b) Implement the logic with a CMOS implementation.
- (c) How many transistors are required in the CMOS implementation?
- (d) Can you implement the logic with only NAND gates? If so, show the implementation.

(a)

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$D = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= \bar{A}BC + ABC + A\bar{B}C + ABC + AB\bar{C} + ABC$$


$$= (\bar{A} + A)BC + AC(\bar{B} + B) + AB(\bar{C} + C)$$

$$= BC + AC + AB$$

Question 4: [20 Marks]


Consider you need to design a temperature control system for your classroom at BRAC University. Your system has 1 Output **D**, and 3 inputs **A**, **B**, and **C** that come directly from three different sensors installed in the room. When a certain threshold of the temperature is crossed, each sensor gives a logical **HIGH** output. Your logic circuit should turn on the AC (**D = 1**) when the **majority** of inputs are **HIGH**.

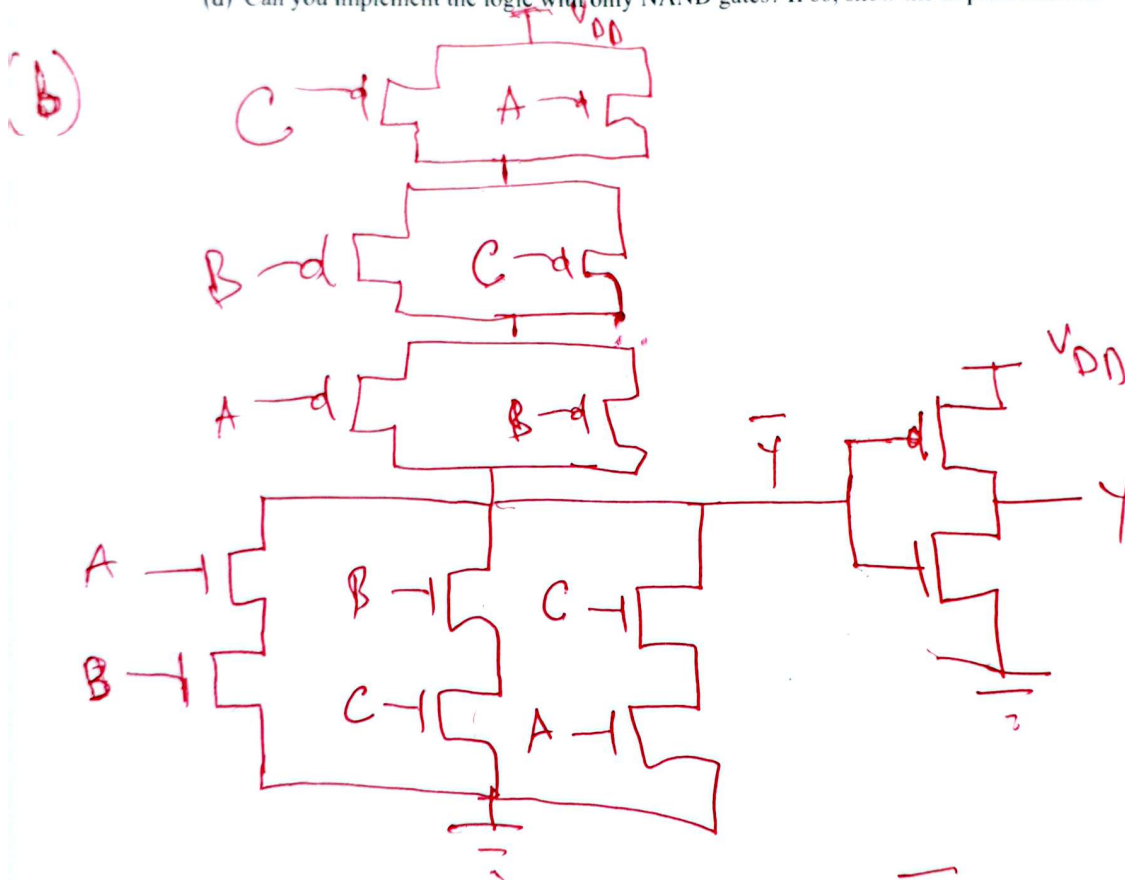- (a) Convert the problem statement into a Truth Table and write the simplified Boolean expression.
- (b) Implement the logic with a CMOS implementation.
- (c) How many transistors are required in the CMOS implementation?
- (d) Can you implement the logic with only NAND gates? If so, show the implementation.



(c) 14

(d) Yes you can.

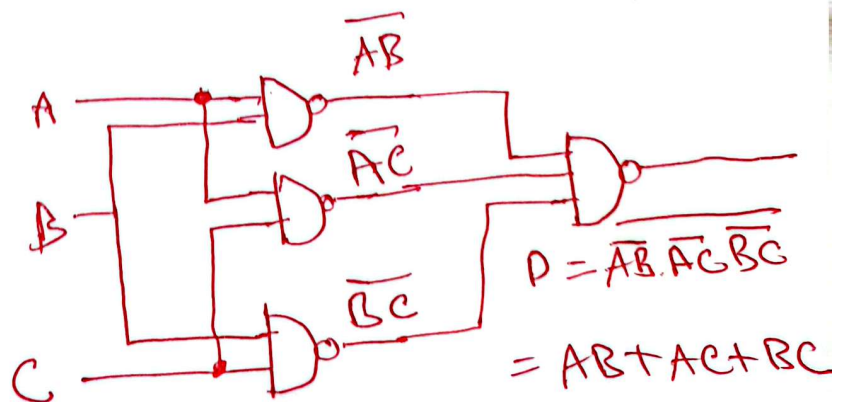

Question 5:[10 Marks]


Imagine a logic circuit with 1 output f , and 4 input lines $d3$, $d2$, $d1$, and $d0$.

- Let's define a 2-bit selector input $S = s1\ s0$
- The output f is determined as follows:

S	f
00	$d3$
01	$d2$
10	$d1$
11	$d0$

- (a) Write the Boolean expression for this logic and implement the circuit using basic gates.
(b) Implement this logic using a 2-to-1 multiplexer.

$$(a) f = \overline{s_0}\overline{s_1}d_3 + \overline{s_0}s_1d_2 + s_0\overline{s_1}d_1 + s_0s_1d_0$$

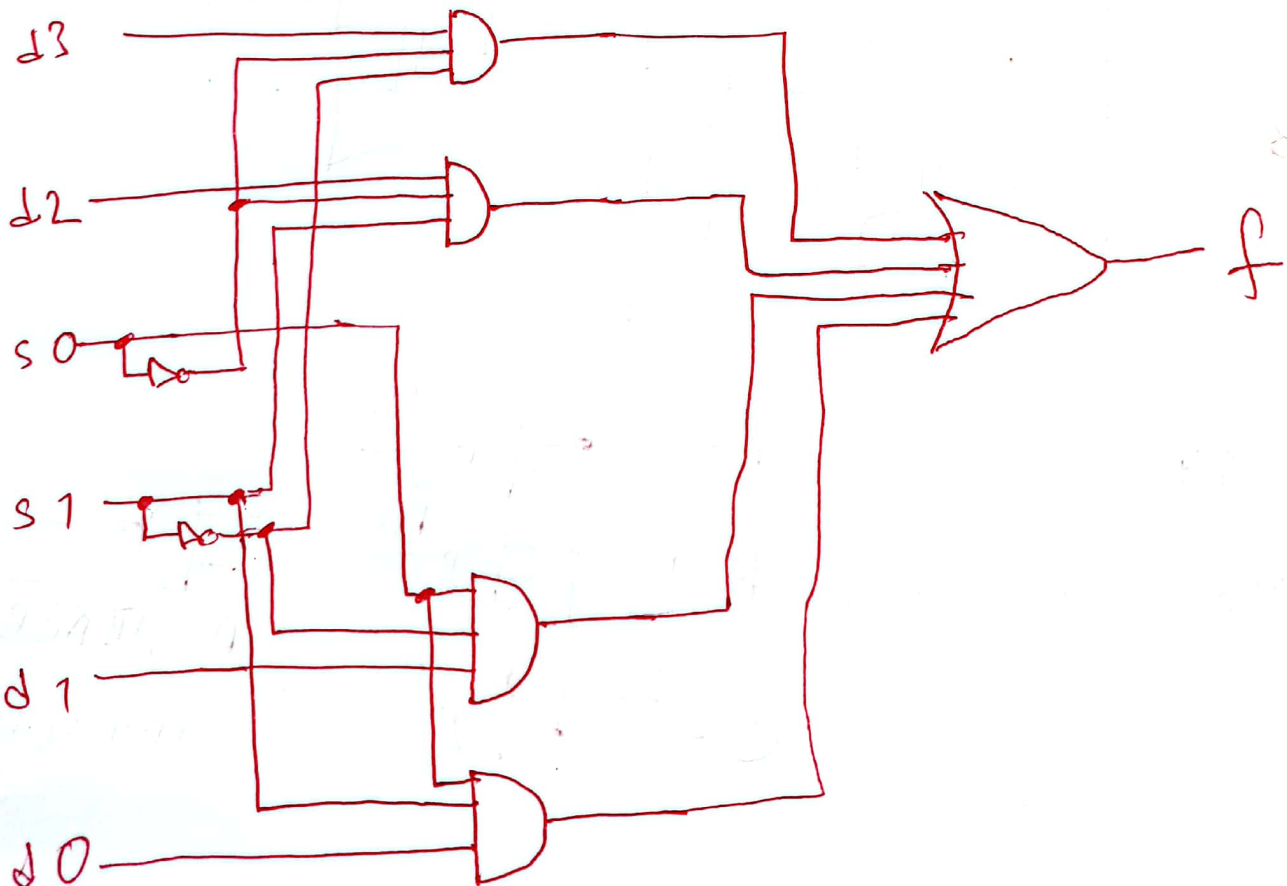

Question 5:[10 Marks]

Imagine a logic circuit with 1 output f , and 4 input lines $d3$, $d2$, $d1$, and $d0$.

- Let's define a 2-bit selector input $S = s1\ s0$
- The output f is determined as follows:

S	f
00	$d3$
01	$d2$
10	$d1$
11	$d0$

- (a) Write the Boolean expression for this logic and implement the circuit using basic gates.
(b) Implement this logic using a 2-to-1 multiplexer.

