


Lecture 7 : Zener Diodes

Outline

- Voltage Regulators
- Forward Bias (FB) Diodes as Voltage Regulators
- Drawbacks of (FB) Diodes as Voltage Regulators
- Diode Breakdown Region
- Zener Diodes – Introduction and analysis
- Zener Diodes as Voltage Regulators
- Practice Problems

Voltage Regulators

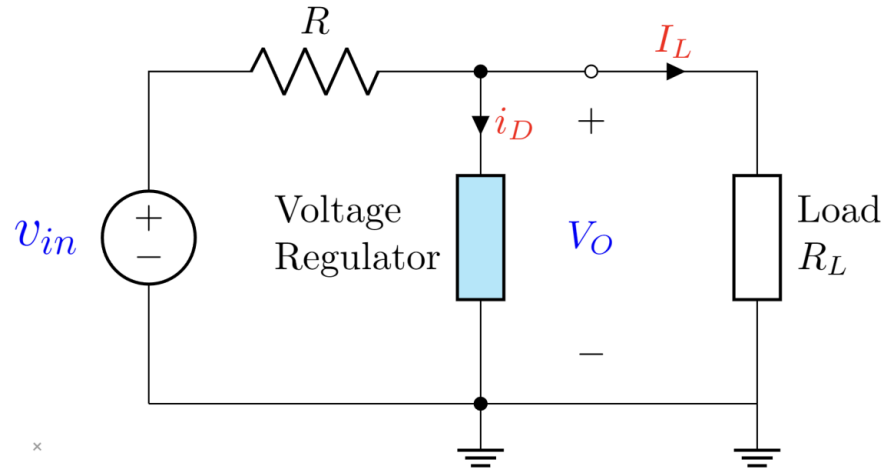- **Voltage Regulation** is the measure of how well a system can provide near constant voltage.
- **Voltage Regulators** provide steady voltage independent of how much power is drawn from the power source




Voltage Regulator:

Tries to maintain a voltage constant at V_O

Voltage Regulators

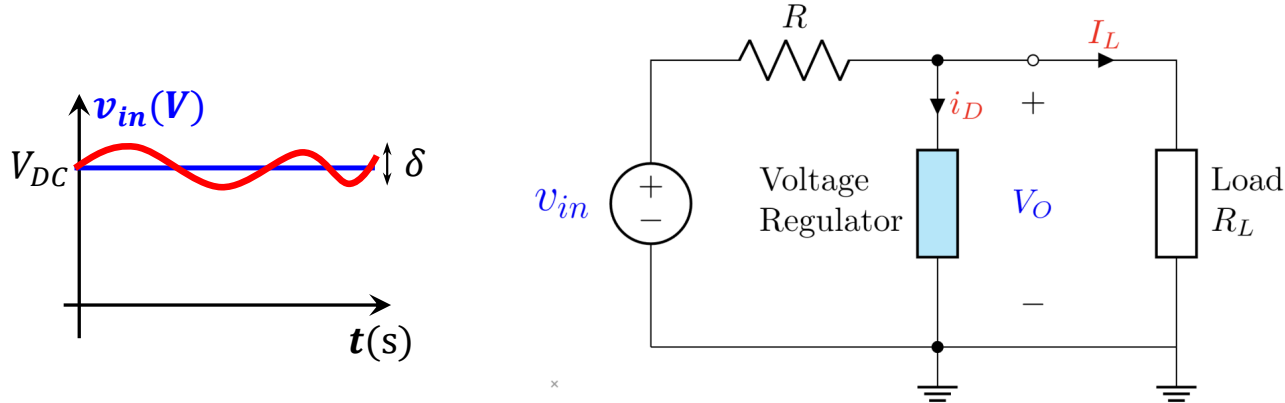Let's assume that v_{in} is not a perfect DC source. It supplies a voltage of $(V_{DC} \pm \delta)$ V



Voltage Regulator:

Tries to maintain a voltage constant at V_O even when v_{in} is varying.


Variables: V_O should remain constant irrespective of the changes in the following quantities:

1. **Input Voltage:** v_{in}
2. **Load Current:** I_L
3. **VR current:** i_D

Voltage Regulator – Worst Case Scenario

Worst Case Scenario occurs when the three variables (v_{in} , I_L , and i_D) change in such a way, such that maintaining V_O constant requires the most power (current) from the **Voltage Regulator**.

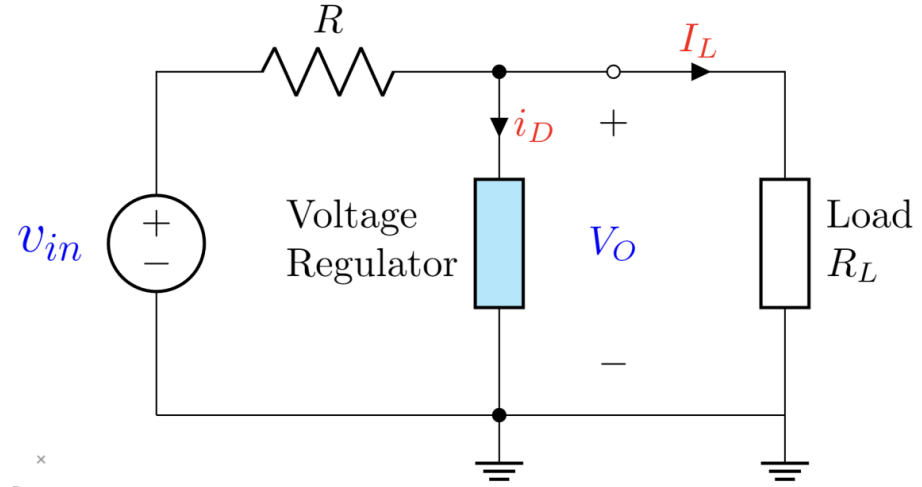The **Voltage regulator** is at its maximum capacity at the worst case.



Worst Case Scenario occurs when

1. **Input Voltage is minimum:** $v_{in}(\min)$
2. **Load Current is maximum:** $I_L(\max)$
3. **VR current minimum:** $i_D(\min)$

Practice Problem 1

The circuit of the adjacent **Figure** is specified to have the following parameters. The supply voltage V_{in} is nominally 3 V but can vary by ± 0.1 V. R_L can draw a maximum of 10 mA and $i_D(\min) = 1$ mA.


What is R for worst case scenario if v_D (V_O) is to be regulated at 0.6 V? [Since r_o is not provided, you can consider the CVD model.]

Solution:

Worst Case Scenario occurs when

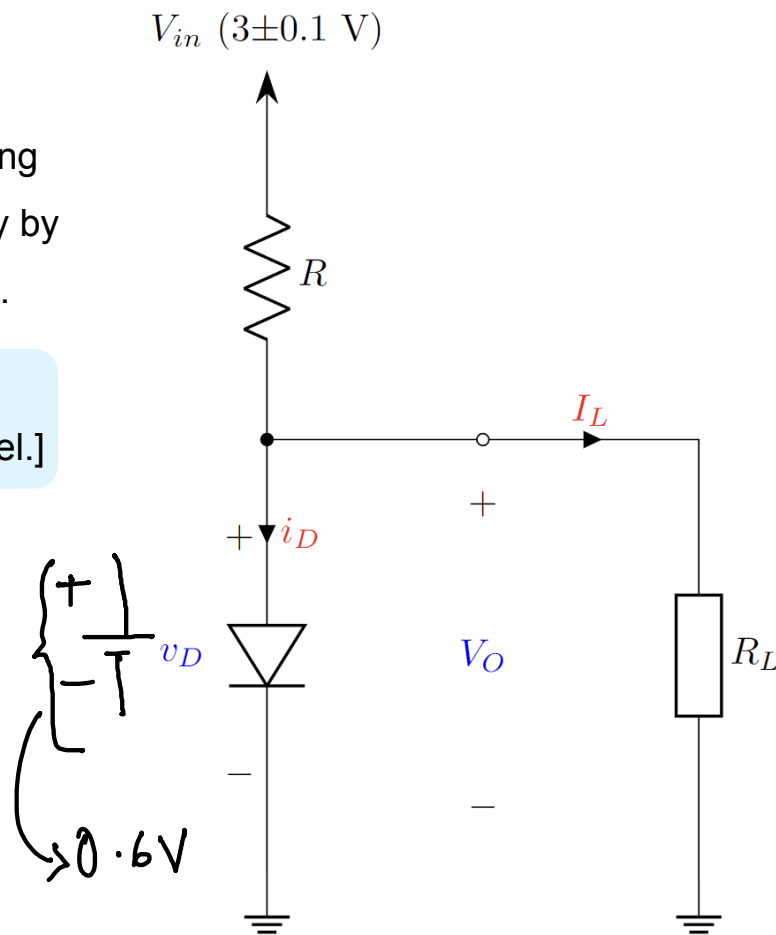1. $v_{in}(\min) = 3 - 0.1 \text{ V} = 2.9 \text{ V}$
2. $I_L(\max) = 10 \text{ mA}$
3. $i_D(\min) = 1 \text{ mA}$

$$\frac{V_{in}(\min) - 0.6}{R} = I_L(\max) + i_D(\min)$$



Practice Problem 1


The circuit of the adjacent **Figure** is specified to have the following parameters. The supply voltage V_{in} is nominally 3 V but can vary by ± 0.1 V. R_L can draw a maximum of 10 mA and $i_D(\min) = 1$ mA.

What is R for worst case scenario if v_D (V_O) is to be regulated at 0.6 V? [Since r_o is not provided, you can consider the CVD model.]

Solution:
$$\frac{V_{in}(\min) - 0.6}{R} = I_L(\max) + i_D(\min)$$


$$R = \frac{2.9 - 0.6}{10 - 1} \text{ k}\Omega = 0.209 \text{ k}\Omega$$

$$\therefore R = 209 \Omega$$

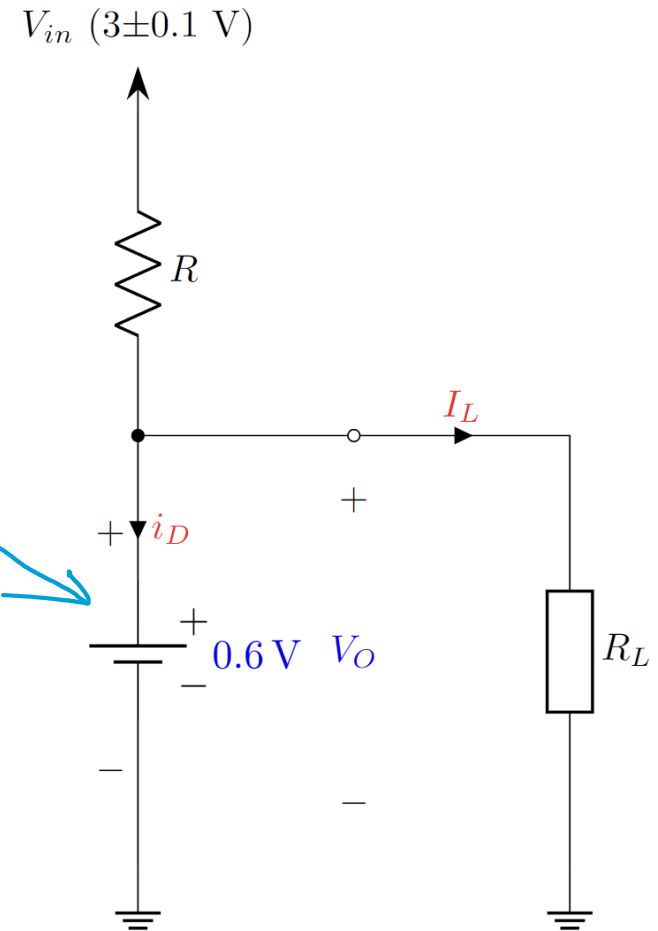

Drawbacks of Diodes as Voltage Regulators

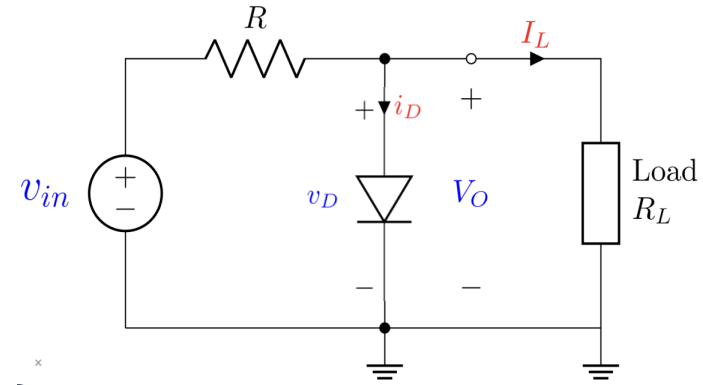
- Regulation voltage is low: $\sim V_{D0}$ (0.3 ~ 1 V)
- High i_D (min)
- R can be low \rightarrow High power loss




Possible Solution:

Stacked Diodes in Series: -- Regulation Voltage can be increased to $n \cdot V_{D0}$ for n stacked diodes.

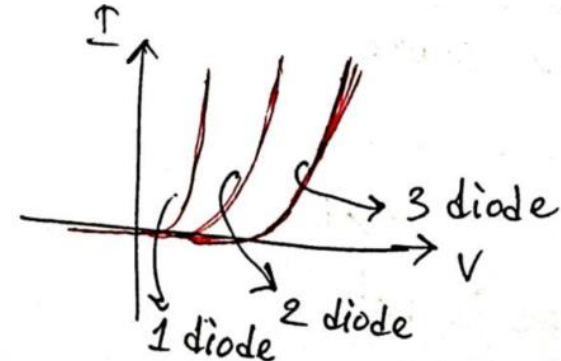However, this can make the diodes deviate more from ideal model. **IV characteristics** become flatter (more lossy).





Zener Diode IV

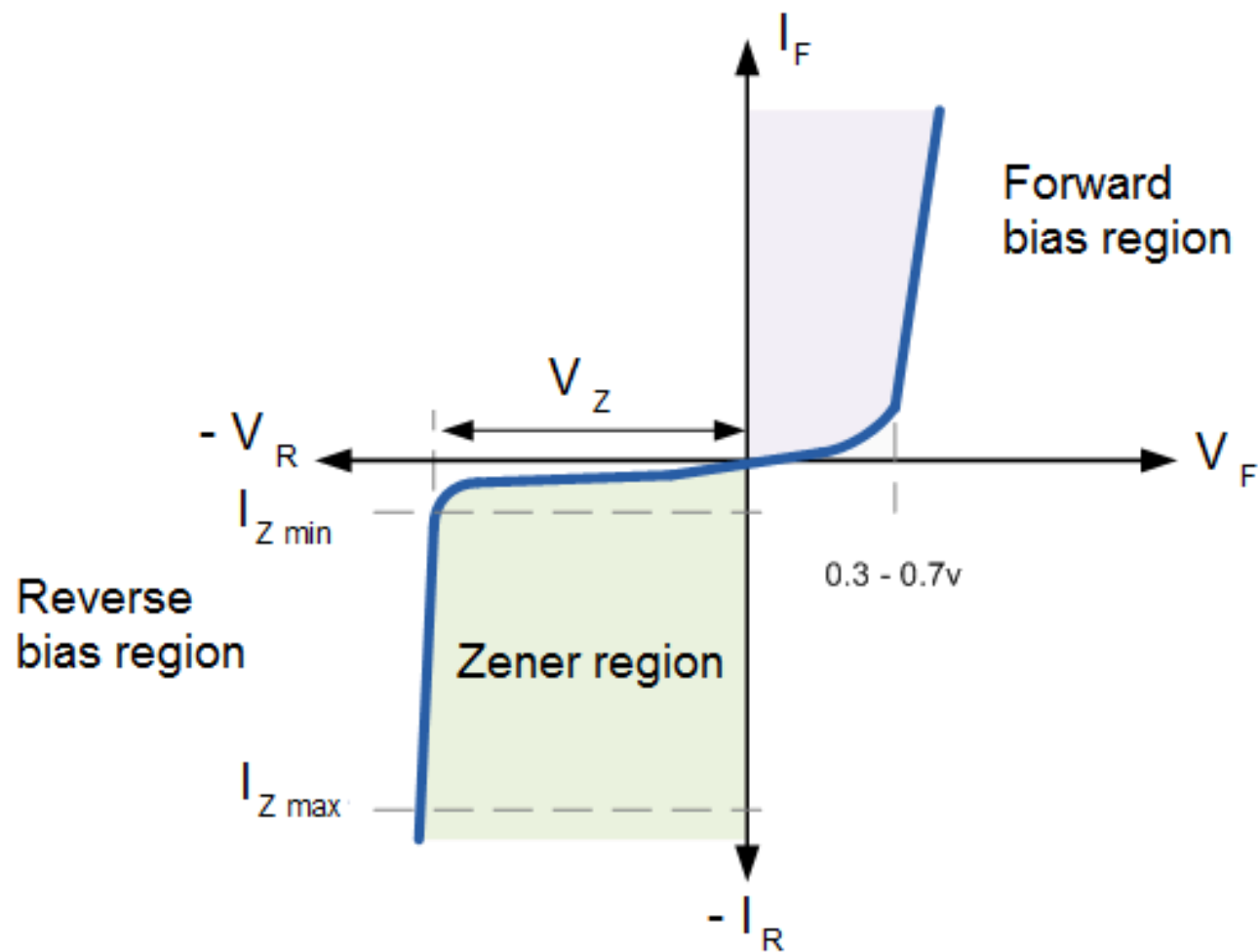

Zener Diode IV

Breakdown Region ($V_Z > V_{Z0} \approx V_{ZK}$)


$$V_Z = V_{Z0} + I_Z r_z$$

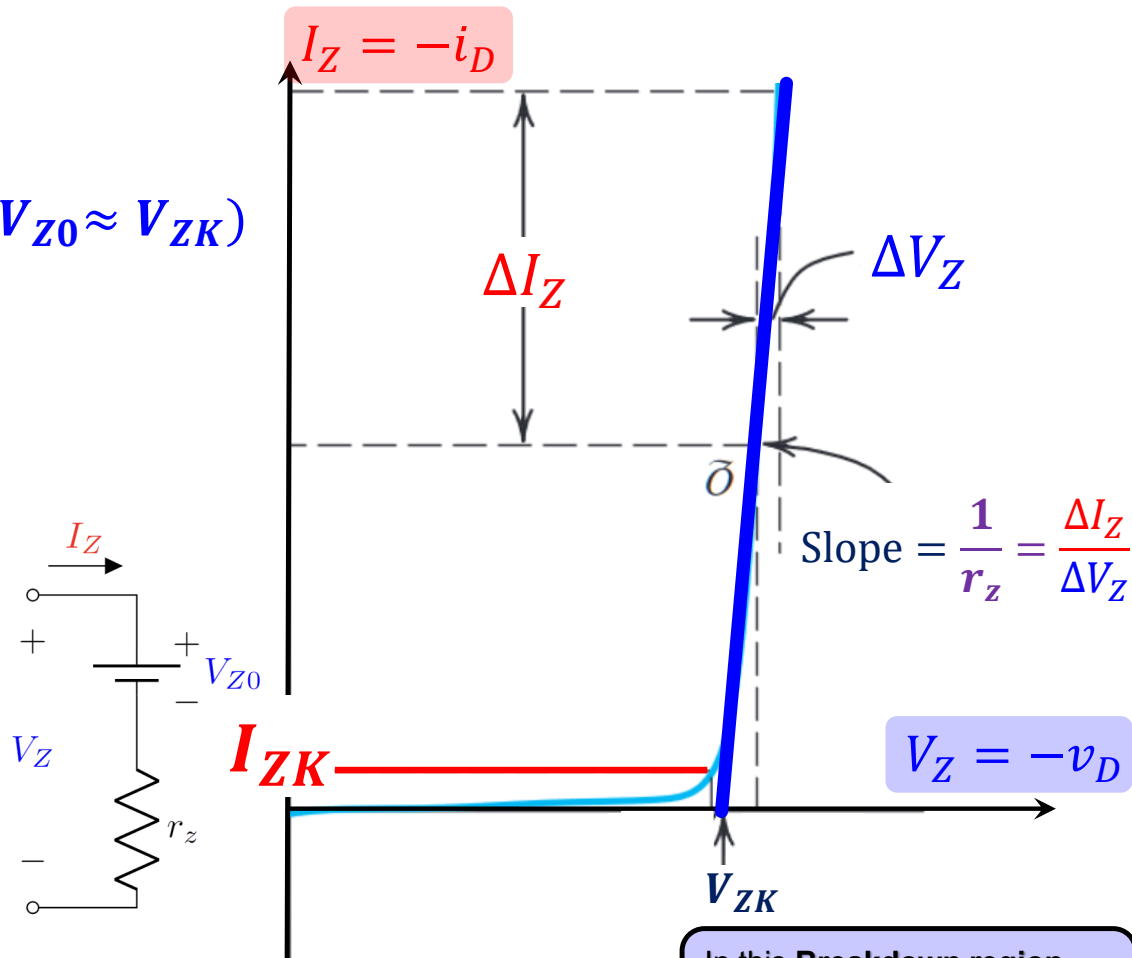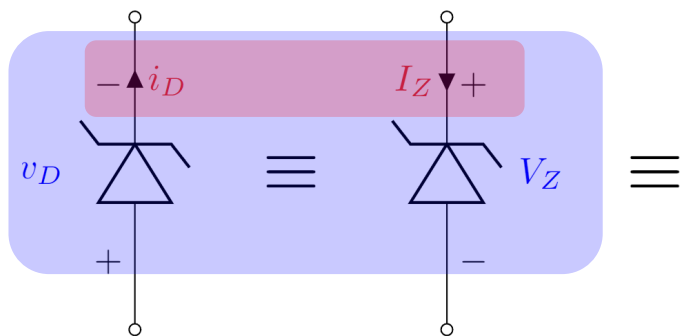

In this **Breakdown region**, the diode acts almost like a “constant voltage source”.


Zener Diode Breakdown IV Characteristic

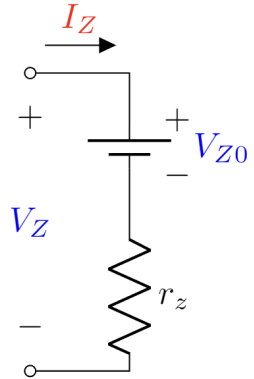Breakdown Region ($V_Z > V_{Z0} \approx V_{ZK}$)



$$V_Z = V_{Z0} + I_Z r_z$$

$$I_Z = I_{ZK}$$

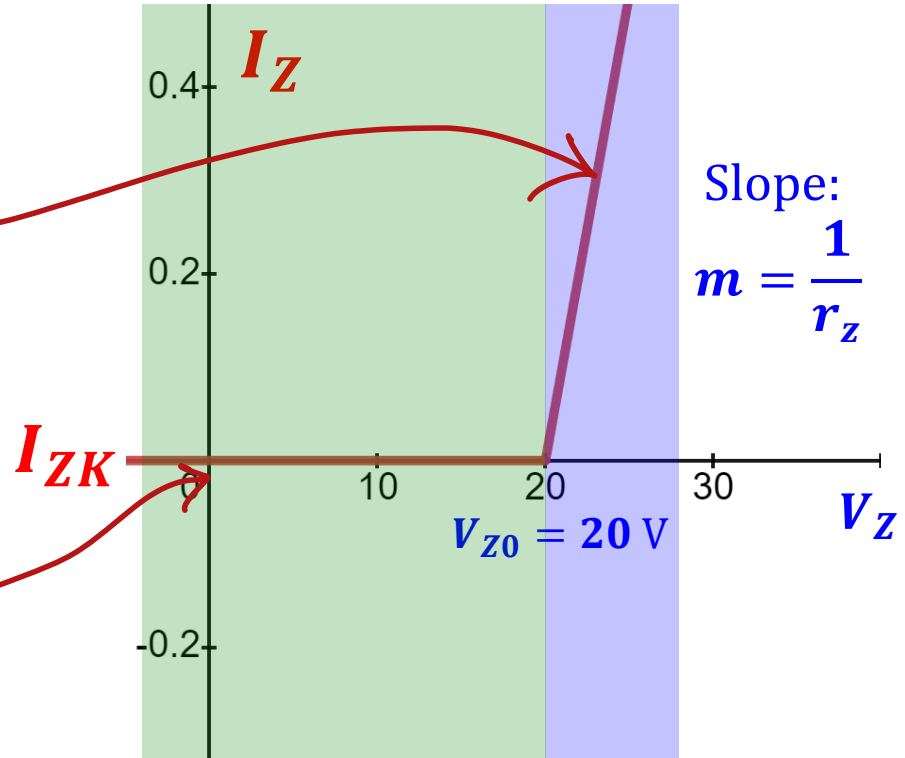

V_Z : Total RB Voltage Across **Zener** diode

V_{Z0} : Zener knee voltage

Practice Problem 2

The 6.8 V Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1\text{ V}$.


$$V^+ = 10 \pm 1\text{ V}$$

$$V_Z = 6.8\text{ V at } I_Z = 5\text{ mA}$$

$$r_z = 20\ \Omega.$$

$$I_{ZK} = 0.2\text{ mA}.$$


- Find V_O with no load and with V^+ at its nominal value
- (For $R_L = 0.5\text{ k}\Omega$). Find the I_Z . In this scenario, calculate the Zener voltage V_O , load current I_L and input current I
- Find the R_L that would give rise to worst-case scenario at worst case V^+ . In this worst-case scenario, calculate the Zener voltage V_Z , load current I_L and input current I
- (For $R_L = 2\text{ k}\Omega$). Find the I_Z . In this scenario, calculate the Zener voltage V_O , load current I_L and input current I
- Design the circuit, i.e., find the minimum value of the input voltage V^+ such that, voltage regulation is maintained even in the worst-case scenario for $R_L = 2\text{ k}\Omega$. (Forget that V^+ is 10 V)
- Determine whether the circuit will maintain regulation if V^+ is increased. If yes, argue if it should be increased or not.

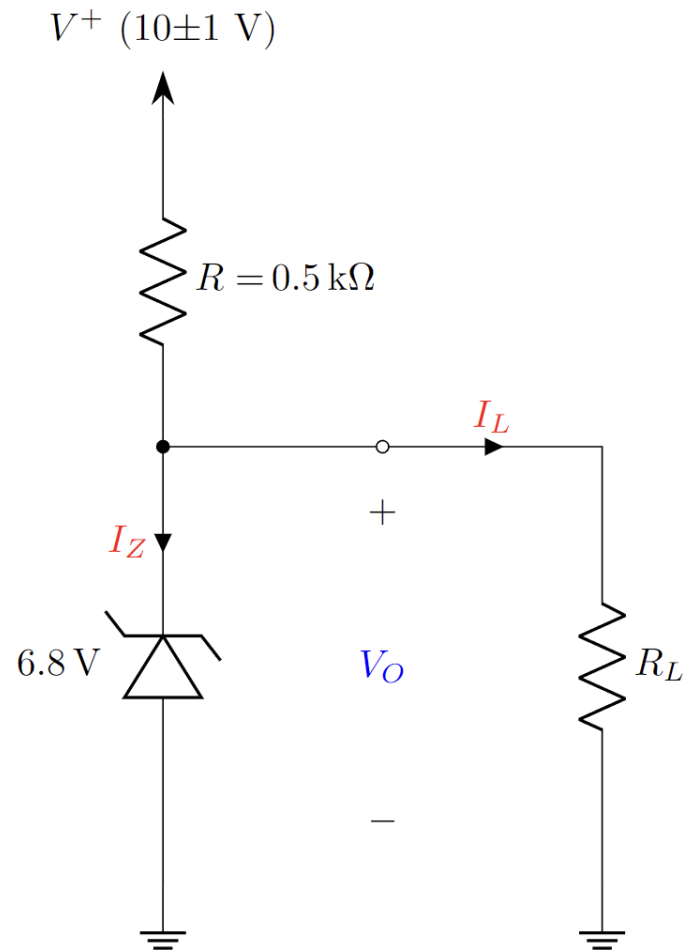

Practice Problem 2

The 6.8 V Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1\text{ V}$.

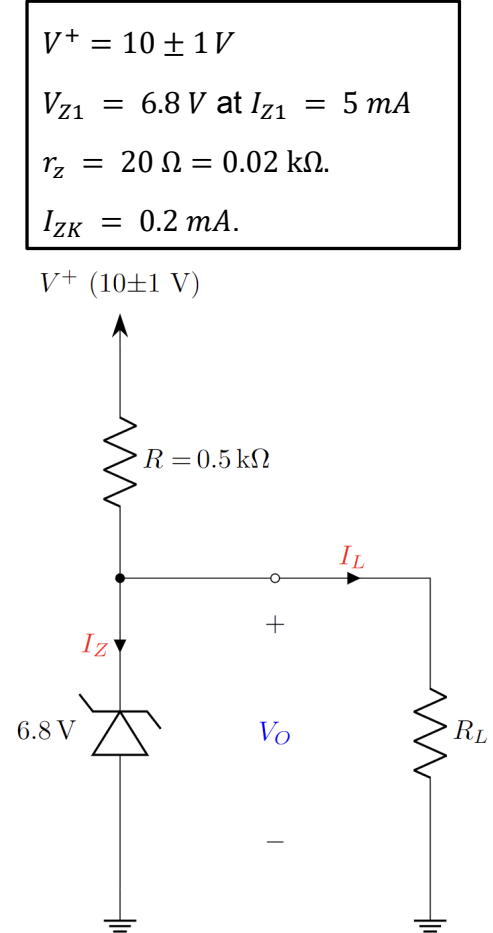- (a) Find V_0 with no load and with V^+ at its nominal value



Practice Problem 2

The 6.8 – V Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage V^+ is nominally 10 V but can vary by ± 1 V.

(a) Find V_o with no load and with V^+ at its nominal value

Solution:


Extracting Zener diode 's reverse cut-in voltage

$$V_{ZO} = 6.8 - 5 \times 0.02 \text{ V}$$

$$\therefore V_{ZO} = 6.7 \text{ V}$$

Determining current from the 10 V source
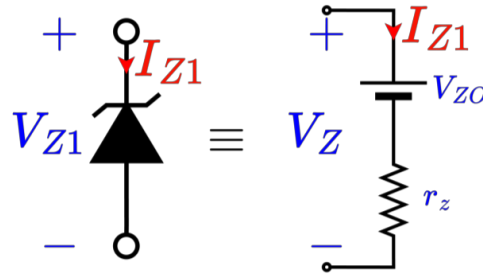
$$I = \frac{10 - 6.7}{0.5 + 0.02} \text{ mA} = 6.346 \text{ mA}$$



Determining output voltage

$$V_o = 6.7 + 6.346 \times 0.02 \text{ V}$$


$$V_o = 6.82692 \text{ V}$$

$$V^+ = 10 \pm 1 \text{ V}$$

$$V_{Z1} = 6.8 \text{ V at } I_{Z1} = 5 \text{ mA}$$

$$r_z = 20 \Omega = 0.02 \text{ k}\Omega.$$

$$I_{ZK} = 0.2 \text{ mA}.$$

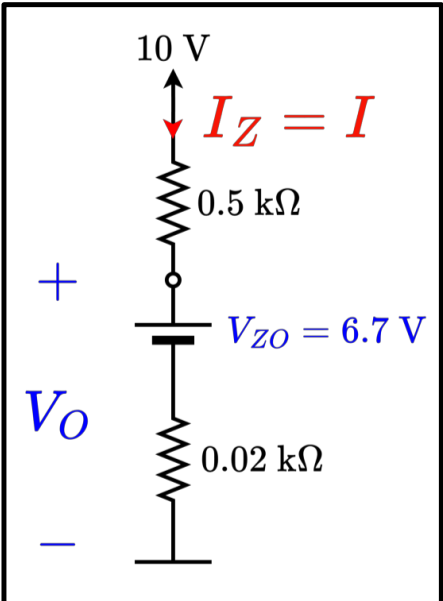

Practice Problem 2

The 6.8 V Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1\text{ V}$.

(b) (For $R_L = 0.5\text{ k}\Omega$). Find the I_Z . In this scenario, calculate the Zener voltage V_O , load current I_L and input current I

Solution:


$$V^+ = 10 \pm 1\text{ V}$$

~~$$V_Z = 6.8\text{ V at } I_Z = 5\text{ mA}$$~~

$$V_{ZO} = 6.7\text{ V}$$

$$r_Z = 20\ \Omega.$$

$$I_{ZK} = 0.2\text{ mA}.$$

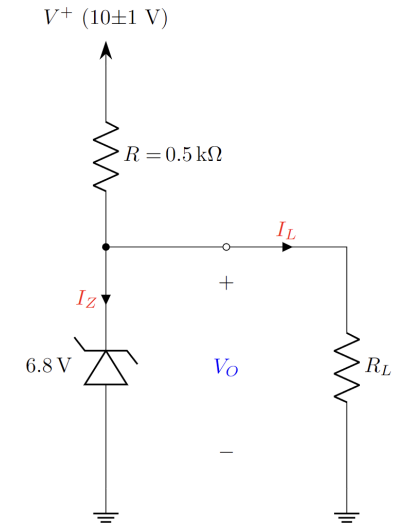

Practice Problem 2

The 6.8 V Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1\text{ V}$.

(b) (For $R_L = 0.5\text{ k}\Omega$). Find the I_Z . In this scenario, calculate the Zener voltage V_O , load current I_L and input current I

Solution:

Solving the node equation at V_O .

$$\frac{(10 \pm 1) - V_O}{R} = \frac{V_O - V_{ZO}}{r_z} + \frac{V_O}{R_L}$$

$$\frac{(10 \pm 1) - V_O}{0.5} = \frac{V_O - 6.7}{0.02} + \frac{V_O}{0.5}$$

$$\therefore V_O = 6.537 \sim 6.611\text{ V}$$

As, $V_O < V_{ZO}$, the Zener diode will be in cut off

$$I_Z = 0$$


$$V^+ = 10 \pm 1\text{ V}$$

~~$$V_Z = 6.8\text{ V at } I_Z = 5\text{ mA}$$~~

$$V_{ZO} = 6.7\text{ V}$$

$$r_z = 20\ \Omega.$$

$$I_{ZK} = 0.2\text{ mA}.$$

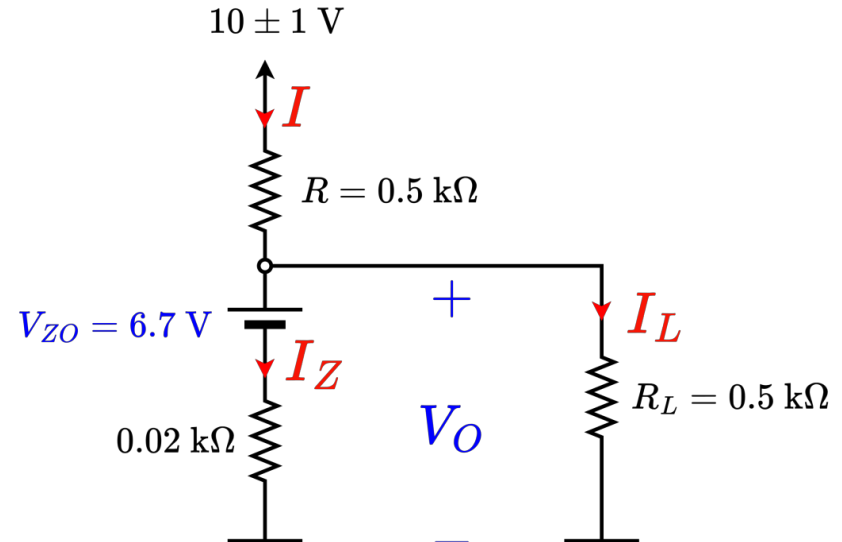

Practice Problem 2

The 6.8 – V Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage V^+ is nominally 10 V but can vary by ± 1 V.

(b) (For $R_L = 0.5 \text{ k}\Omega$). Find the I_Z . In this scenario, calculate the Zener voltage V_O , load current I_L and input current I

Solution:

$$V^+ = 10 \pm 1 \text{ V}$$

$$V_Z = 6.8 \text{ V at } I_Z = 5 \text{ mA}$$

$$V_{ZO} = 6.7 \text{ V}$$

$$r_Z = 20 \Omega.$$


$$I_{ZK} = 0.2 \text{ mA}.$$

So,

$$V_O = \frac{10 \pm 1}{2} \text{ V} = 5 \pm 0.5 \text{ V}$$

$$I_Z = 0 \text{ mA}$$
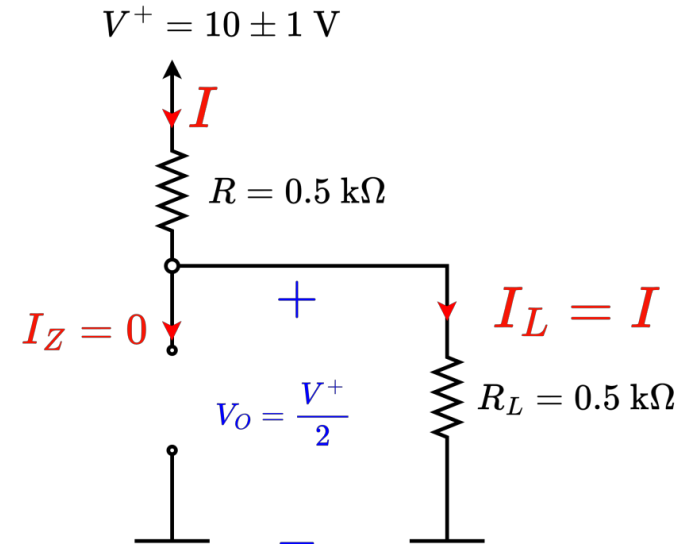
$$I_L = \frac{V^+ \pm 1}{R + R_L} = \frac{10 \pm 1}{1} \text{ mA} = 10 \pm 1 \text{ mA}$$



(c) Find the R_L that would give rise to worst-case scenario at worst case V^+ . In this worst-case scenario, calculate the Zener voltage V_Z , load current I_L and input current I


(c) The determining factor for worst-case scenario:

$$I_Z \geq I_{ZK}$$

$$\therefore \text{At } I_Z = I_{ZK} \text{ mA}$$

$$V_o = V_{Z0} + I_{ZK} r_z = 6.704 \text{ V}$$


$$\therefore I = I_L + I_{ZK}$$

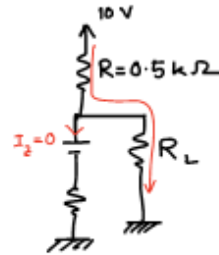

$$\frac{10 - V_o}{0.5 \text{ k}} = \frac{V_o}{R_L} + I_{ZK}$$

$$\Rightarrow \frac{10 - 6.704}{0.5 \text{ k}} = \frac{6.704}{R_L} + 0.2 \text{ mA}$$

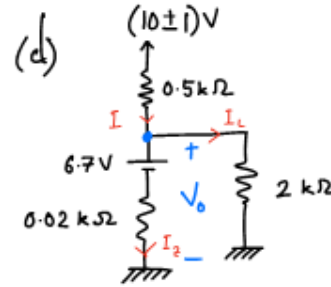(d) (For $R_L = 2 \text{ k}\Omega$). Find the I_Z . In this scenario, calculate the Zener voltage V_o , load current I_L and input current I



$$I = I_Z + I_L$$

$$\frac{V^+ - V_o}{R} = \frac{V_o - V_{Z0}}{r_z} + \frac{V_o}{R_L}$$


$$\Rightarrow V_o \left(\frac{1}{R} + \frac{1}{r_z} + \frac{1}{R_L} \right) - V_{Z0} \left(\frac{1}{r_z} \right) = \frac{V^+}{R}$$

$$\Rightarrow V_o \left(\frac{1}{0.5} + \frac{1}{2} + \frac{1}{0.02} \right) - V_{Z0} \left(\frac{1}{0.02} \right) = \frac{10}{0.5}$$


$$\Rightarrow V_o = \frac{355}{54} \text{ V} = 6.76 \text{ V}$$

$$I_Z = \frac{V_o - V_{Z0}}{r_z} = \frac{6.76 - 6.7}{0.02} = 3.1 \text{ mA} > I_{ZK}$$

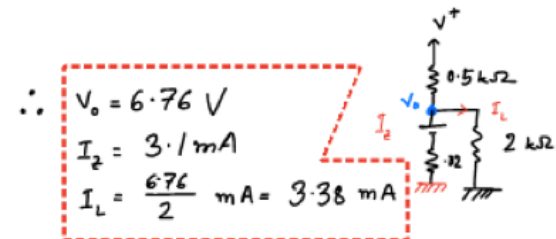So, the zener diode can sustain this load.



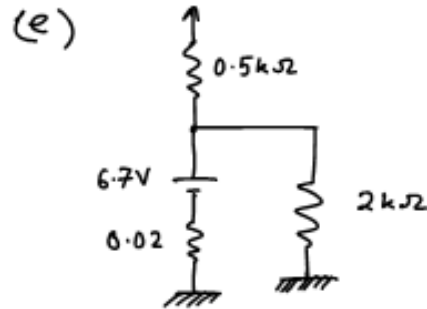(e) Design the circuit, i.e., find the minimum value of the input voltage V^+ such that, voltage regulation is maintained even in the worst-case scenario for $R_L = 2 \text{ k}\Omega$. (Forget that V^+ is 10 V)



At worst case: $I_2 = I_{2k}$

$$\therefore V_o = V_{z0} + I_{2k} r_z$$

$$= 6.7 + 0.2 \times 0.02 = 6.704 \text{ V}$$

For $R_L = 2 \text{ k}\Omega$

$$I_L = \frac{6.704}{2} = 3.352 \text{ mA}$$



$$I = I_L + I_{2k}$$

$$I = 3.552 \text{ mA}$$

$$\therefore V^+ \geq V_o + IR$$

$$V^+ \geq 8.48 \text{ V}$$

Solving Problems

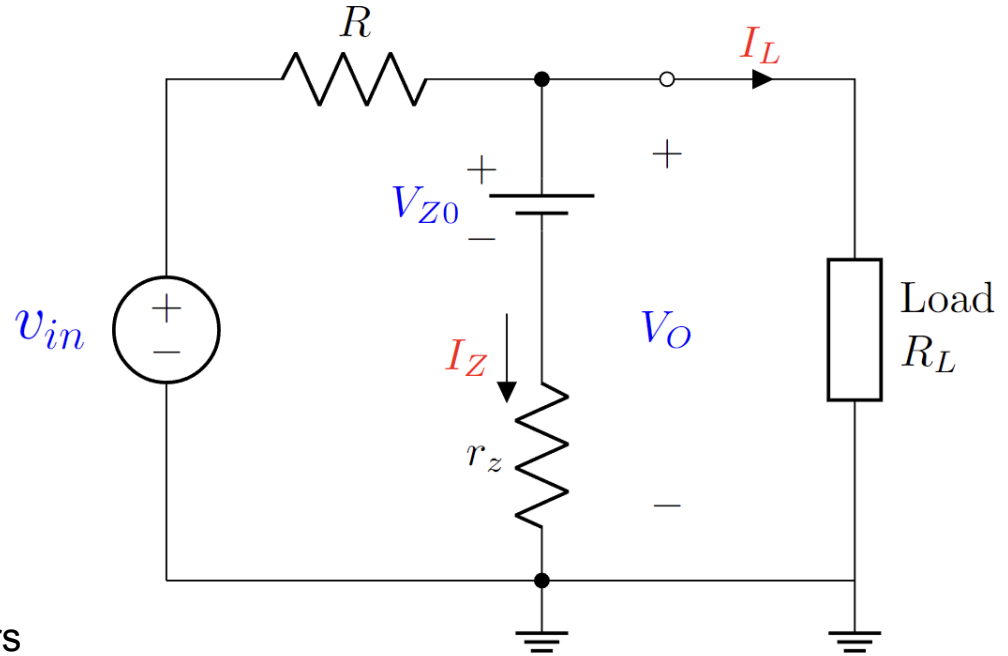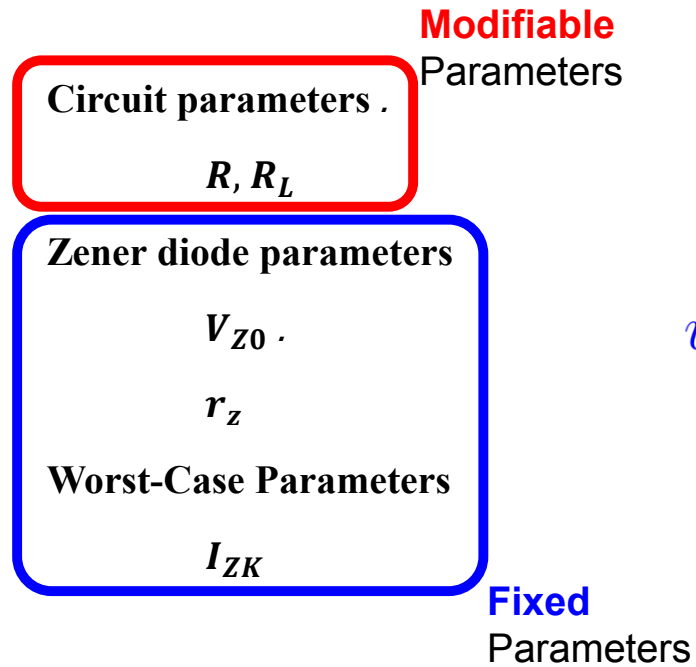

Obtain the Fixed Parameters first


$$V_O = V_{ZO} + I_Z r_z$$

$$I_Z = \frac{V_O - V_{ZO}}{r_z}$$

KCL/Nodal Analysis at node V_O

$$\frac{v_{in} - V_O}{R} = I_Z + \frac{V_O}{R_L}$$
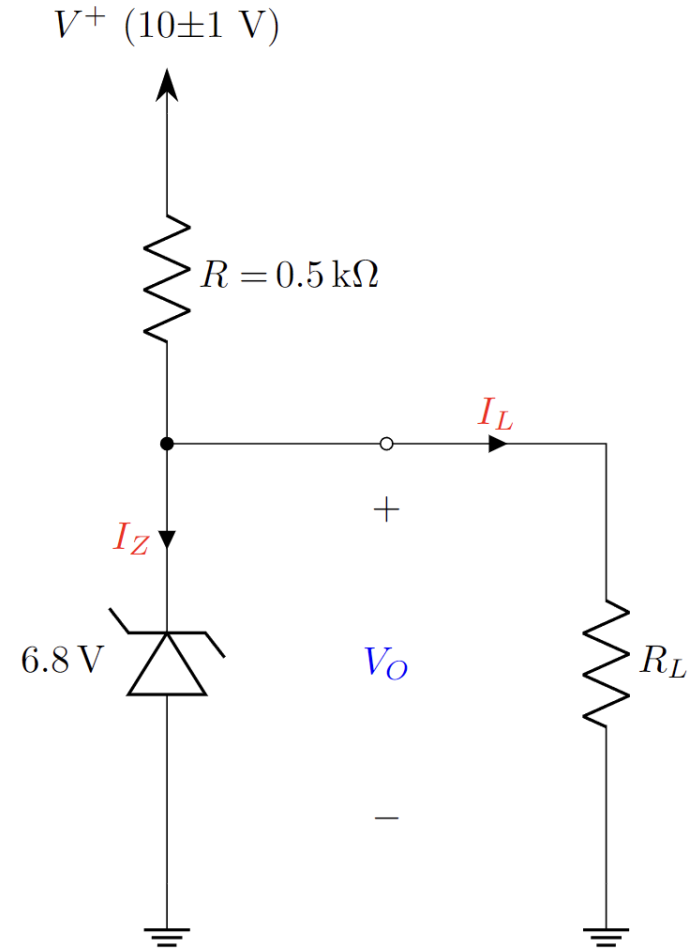
$$\frac{v_{in} - V_O}{R} = \frac{V_O - V_{ZO}}{r_z} + \frac{V_O}{R_L}$$



Practice Problem 3

The Zener diode in the circuit of **Figure** is specified to have the following parameters. The **supply voltage** V_{in} is nominally 5 V but can vary by $\pm 10\%$.

Load current can vary from 0 mA to 50 mA.


$$V_{in} = 5\text{ V} \pm 10\%$$

$$V_{Z0} = 3\text{ V}$$

$$r_z = 0\ \Omega$$

$$I_{ZK} = 1\text{ mA.}$$

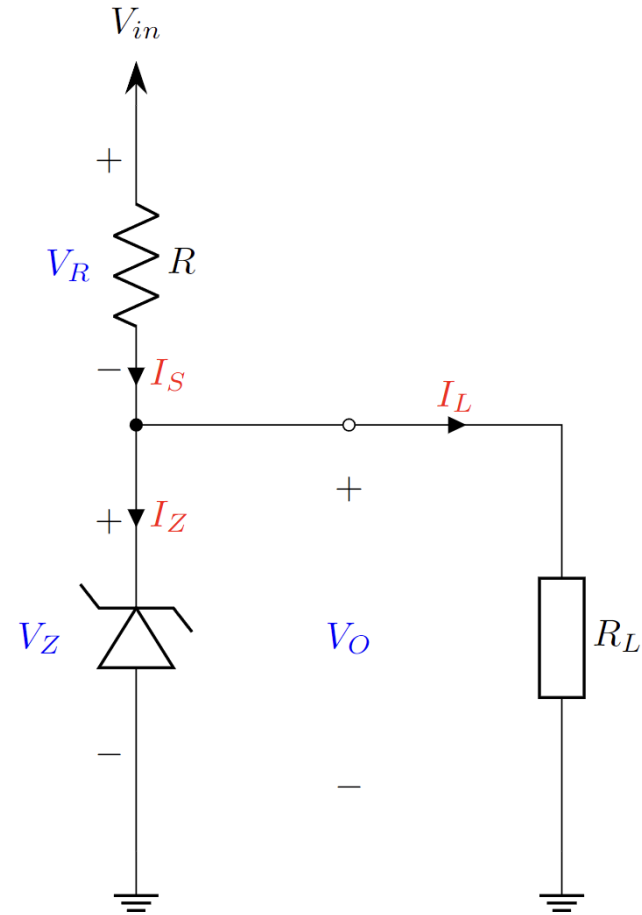- Find **minimum and maximum input Voltage, $V_{in}(\text{min})$ and $V_{in}(\text{max})$, maximum and minimum load current $I_L(\text{max})$ and $I_L(\text{min})$, minimum diode current $I_Z(\text{min})$.**
- Find the I_Z , V_{in} and I_L at worst-case scenario.
- For worst case what is I_S and V_R .
- Find R for which diode maintains regulation at worst case scenario



Practice Problem 4


The Zener diode in the circuit of **Figure** is specified to have the following parameters.

$$V_{Z0} = 3 \text{ V}$$

$$r_z = 20 \, \Omega, 0 \, \Omega$$

$$I_{ZK} = 1 \text{ mA.}$$

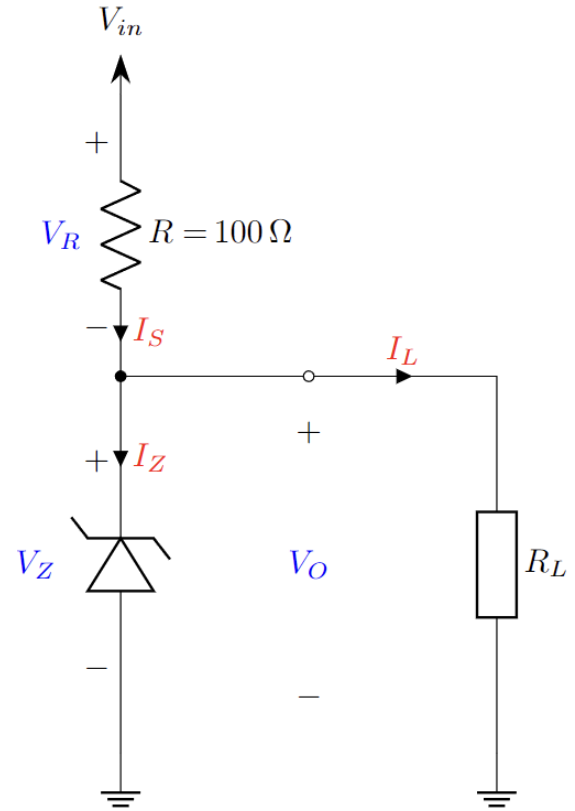- a) Find **minimum input voltage, $V_{in}(\min)$** for which the diode maintains regulation, when $R_L = 10 \text{ k}\Omega$.
- b) Find worst case R_L if the **input voltage V_{in}** is nominally 5 V but can vary by $\pm 10 \%$



Some important tips

- If V_{ZK} , V_{ZO} and r_z are given, we can calculate $I_{ZK} = \frac{V_{ZK} - V_{ZO}}{r_z}$
- If V_{ZO} and r_z are **not** provided, consider $V_{ZK} = V_Z = V_{ZO}$
- Consider $I_{ZK} = 0$ if not provided

