


CSE 260: Digital Logic Design
Md. Arifur Rahman [MAR]

Semester: **Fall 2022**
Full Marks: **10**

- For Q 1-3, refer to: <https://youtu.be/EkS5kauNIBQ>

- [illegible]

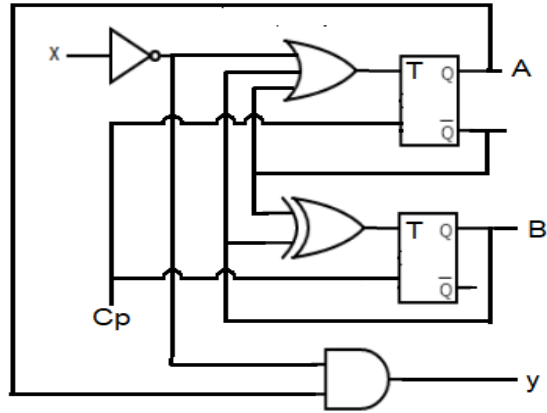5. Draw the state diagram for the given circuit.



For Q 4-5, refer to:

Sequential Circuit to State Diagram Examples

Example 1: <https://youtu.be/SmiIClU07jc> (buX)

Bengali: https://youtu.be/9D_h2UsQ6xY (buX)

Example 2 (English): <https://youtu.be/mtnKKDgcrag> (buX)

End of Assignment 4 (Quiz 4 Syllabus)
