

CSE 260: Digital Logic Design

Lab Report

Experiment Name: Universal Gates and Applications
of Boolean algebra

Submitted By :

Group No : 05

Name : Jannatul Somiya Mahmud (22101698)

Umme Hunna Maryam (22101565)

Mithila Farzana Mila (22101709)

Section : 22

Name of the Experiment: Universal Gates and Applications of Boolean algebra.

Objective:

- ▣ To investigate the rules of Boolean algebra.
- ▣ To gain experience working with practical circuits.
- ▣ To simplify a complex function using Boolean algebra.

Required Components and Equipments:

- ▣ AT-700 Portable Analog / Digital Laboratory
- ▣ IC-7400 (NAND)
- ▣ wires
- ▣ Breadboard

Experimental Setup :

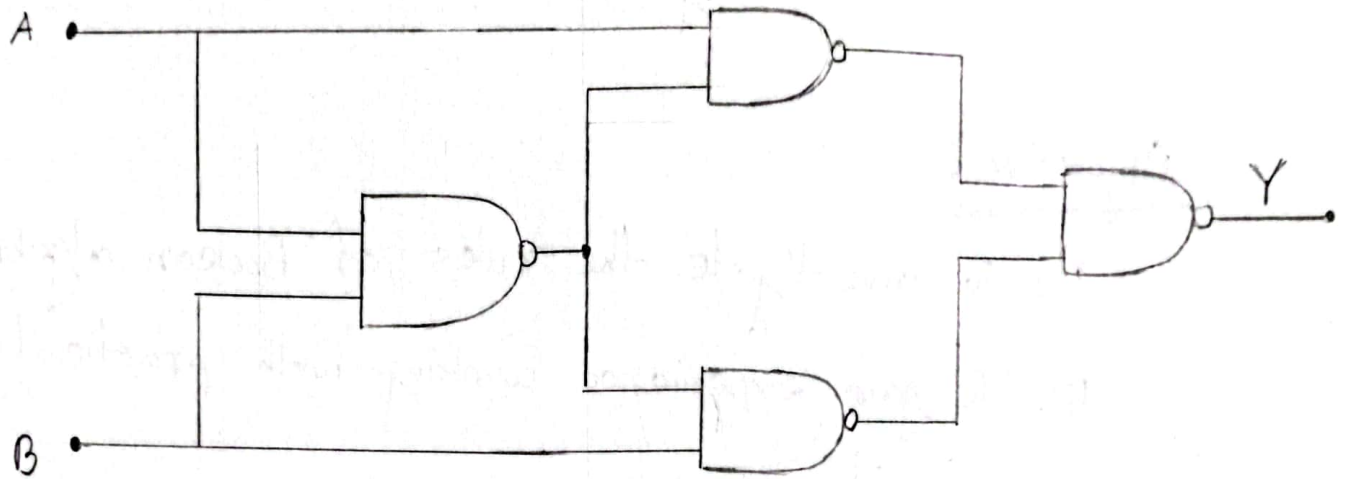


Fig: Building Circuit using Universal Gates (NAND)

Truth Table

Input				Output
A	B	$\bar{A}$	$\bar{B}$	
0	0	1	1	0
1	1	0	0	0
1	0	0	1	1
0	1	1	0	1

Solving the equation:-

$$Y = (\bar{A} + (AB)) \cdot (\bar{B} + (AB))$$

$$\Rightarrow (\bar{A} + (AB)) + (\bar{B} + (AB))$$

$$\Rightarrow \bar{A} \cdot (\bar{A}B) + \bar{B} \cdot (A\bar{B})$$

$$\Rightarrow A \cdot (\bar{A} + \bar{B}) + B \cdot (\bar{A} + \bar{B})$$

$$\Rightarrow (\bar{A} + \bar{B}) \cdot (A + B)$$

$$\Rightarrow A \cdot \bar{A} + \bar{A}B + A\bar{B} + B\bar{B}$$

$$Y \Rightarrow \bar{A}B + A\bar{B}$$

Alk
19.10.22

$\therefore$ The truth table and the equation implies that the setup shown above acts like a XOR gate.

Discussion : 0

During the experiment, we made 4 NAND gates using 1 IC. Each of it has 2 inputs and after solving the circuit, we got the equation for the output,

$$Y = \overline{(A \cdot (\overline{AB})) \cdot (B (\overline{AB}))}$$

Simplifying it, ~~we~~ the final outcome is $\bar{A}B + A\bar{B} = A \oplus B$; which is a X-OR gate

For the gate, we connected the IC vertically on the e-f column of the breadboard. Inserting ~~pin~~ pin 14 with +5V and pin 7 with ground and used wires to input-output segment. The

That's how, using 4 universal gates (NAND) we got to know the practical applications of Boolean algebra mechanism and came with the output of X-OR gate ~~exp~~ expressing the whole algebraic equation and Truth Table as well.