


MSI Circuits

Useful MSI circuits

- Four common and useful MSI circuits are:

- ❖ Decoder
- ❖ Demultiplexer
- ❖ Encoder
- ❖ Multiplexer

- Block-level outlines of MSI circuits:

 


Decoders

- Convert binary information from n input lines to (max. of) 2^n output lines.
- Known as n -to- m -line decoder, or simply $n:m$ or $n \times m$ decoder ($m \leq 2^n$).
- May be used to generate 2^n (or fewer) minterms of n input variables.

Decoders

 - Example: if codes 00, 01, 10, 11 are used to identify four light bulbs, we may use a 2-bit decoder:



- This is a 2×4 decoder which selects an output line based on the 2-bit code supplied.


- Truth table:

X	Y	F ₀	F ₁	F ₂	F ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Decoders

- From truth table, circuit for 2×4 decoder is:
- Note: Each output is a 2-variable minterm ($X'Y'$, $X'Y$, XY' or XY)


X	Y	F_0	F_1	F_2	F_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

Decoders

- Design a 3×8 decoder **by yourself**.


Solution

 

C	B	A		O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0		0	0	0	0	0	0	0	1
0	0	1		0	0	0	0	0	0	1	0
0	1	0		0	0	0	0	0	1	0	0
0	1	1		0	0	0	0	1	0	0	0
1	0	0		0	0	0	1	0	0	0	0
1	0	1		0	0	1	0	0	0	0	0
1	1	0		0	1	0	0	0	0	0	0
1	1	1		1	0	0	0	0	0	0	0

Decoders

 
- In general, for an n -bit code, a decoder could select up to 2^n lines:



As n input generates 2^n output, which reminds us of canonical SOP, thus a decoder can be used to generate any function

Application of Decoder

 - Example 1: Full adder circuit with decoder (3 x 8 decoder)




$$S(x, y, z) = \Sigma(1, 2, 4, 7)$$

$$C(x, y, z) = \Sigma(3, 5, 6, 7)$$


Demultiplexer

 - Given an input line and a set of selection lines, the demultiplexer will direct data from input to a **selected output line**.
- An example of a 1-to-4 demultiplexer:






Typical Application of a DEMUX

 


Demultiplexer

 - The demultiplexer is actually identical to a decoder with enable. A **decoder with an enable** input can function as a demultiplexer (or demux)
Decoder + enable = demultiplexer
- The selection of a specific output line is controlled by the bit values of 'n'-selection lines.



 4-line-to-16 line Decoder constructed with two 3-line-to-8 line decoders with enables



4-line-to-16 line Decoder constructed with two 3-line-to-8 line decoders with enables


w	x	y	z
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

- When $w=0$, the top decoder is enabled and the other is disabled. The bottom decoder outputs are all 0's, and the top eight outputs generate min-terms 0000 to 0111.
- When $w=1$, the enable conditions are reversed. The bottom decoder outputs generate min-terms 1000 to 1111, while the outputs of the top decoder are all 0's.

$$F(a,b,c,d)=\sum(0,1,3,5,12,13)$$

Implement the above boolean function using


- 3:8 Decoder(s).
- 2:4 Decoder(s).

 

$$F(a,b,c,d)=\sum(0,1,3,5,12,13)$$

Implement the above boolean function using


- 3:8 Decoder(s).
- 2:4 Decoder(s).

 

You have to connect D0,D1,D3,D5,D12
& D13 with OR Gate

Multiplexer

 - A multiplexer is a device which has
 - (i) a number of *input* lines
 - (ii) a number of *selection* lines
 - (iii) one *output* line
- A Multiplexer steers one of 2^n inputs to a single output line, using n selection lines. Also known as a *data selector*.





Multiplexer

- Truth table for a 4-to-1 multiplexer:

I_0	I_1	I_2	I_3	S_1	S_0	Y
d_0	d_1	d_2	d_3	0	0	d_0
d_0	d_1	d_2	d_3	0	1	d_1
d_0	d_1	d_2	d_3	1	0	d_2
d_0	d_1	d_2	d_3	1	1	d_3




S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

  



Typical Application of a MUX

 

Multiplexer

- Output of multiplexer is
“sum of the (product of *data lines* and *selection lines*)”
- Often known as Data selector as it selects one of the many inputs and steers the binary information to the output line.
- Example: the output of a 4-to-1 multiplexer is:


$$Y = I_0.(S_1'.S_0') + I_1.(S_1'.S_0) + I_2.(S_1.S_0') + I_3.(S_1.S_0)$$

Try it yourself

- Draw the internal circuit diagram (logic diagram) of a 4-to-1 multiplexer.

Solution

 
$$Y = I_0.(S_1'.S_0') + I_1.(S_1'.S_0) + I_2.(S_1.S_0') + I_3.(S_1.S_0)$$



(a) Logic diagram

s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

 

(c) Block diagram


Larger Multiplexers

- Larger multiplexers can be constructed from smaller ones.
- An 8-to-1 multiplexer can be constructed from smaller multiplexers like this (from two 4x1 and one 2x1):

S ₂	S ₁	S ₀	Y
0	0	0	I ₀
0	0	1	I ₁
0	1	0	I ₂
0	1	1	I ₃
1	0	0	I ₄
1	0	1	I ₅
1	1	0	I ₆
1	1	1	I ₇

Larger Multiplexers

 - Larger multiplexers can be constructed from smaller ones.
- An 8-to-1 multiplexer can be constructed from smaller multiplexers like this (from two 4x1 and one 2x1):




Larger Multiplexers

- Another implementation of an 8-to-1 multiplexer using smaller multiplexers (four 2x1 and one 4x1):

S₂	S₁	S₀	Y
0	0	0	I ₀
0	0	1	I ₁
0	1	0	I ₂
0	1	1	I ₃
1	0	0	I ₄
1	0	1	I ₅
1	1	0	I ₆
1	1	1	I ₇

Larger Multiplexers

 - Another implementation of an 8-to-1 multiplexer using smaller multiplexers (four 2x1 and one 4x1):




S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

Q: Can we use only 2:1 multiplexers?

Larger Multiplexers

Q: Can we use only 2:1 multiplexers?

 

Try it yourself: Larger Multiplexers

- A 16-to-1 multiplexer can be constructed from only 4-to-1 multiplexers:

Encoder

- Encoder is a digital function that produces a **reverse** operation **of a decoder!**
- It has 2^n input lines and n output lines

Example: Octal-binary encoder

TABLE 5-3
Truth Table of Octal-to-Binary Encoder

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

Example: Octal-binary encoder

 


FIGURE 5-13

Octal-to-binary encoder

There are 8 input variables so there will 2^8 input combination, amongst which in Octal-binary encoder only 8 are useful

Example: Priority Encoder

- Design a priority encoder, which will allow more than one input to exist and encodes only the highest priority input line. For example, 8x3 encoder in a if user give D2 and D7 together, it will allow data of D7 to pass.

Priority Encoder



- Accepts multiple values and encodes them
 - Works when more than one input is active
- Consists of:
 - Inputs (2^n)
 - Outputs
 - when more than one output is active, sets output to correspond to highest input
 - V (indicates whether any of the inputs are active). This helps to show the output when all inputs are 0s
- Selectors / Enable

D3	D2	D1	D0	A1	A0	V
0	0	0	0	x	X	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1


Note: Amongst all 3 input, D2 is highest so output reflects the binary value of 2

Note: V is not really an output, just shows whether there is an active input or not.

Priority Encoder

  

Priority Encoder



 


Boolean Function implementation using MSI

Try it yourself

Using 4:1 MUX design

- AND gate
- OR gate
- NOT gate

   

Try it yourself

a) Built the following function using 8x1 Mux.



$$F = \sum(0, 4, 5)$$

b) Design same thing with 3x8 decoder

c) Try designing it with single 4x1 Mux

Solution

- $F = \sum(0, 4, 5)$

  

Rules: for using smaller mux to build larger equation

If the two minterms in a column are not circled, apply 0 to the corresponding multiplexer input.

If the two minterms are circled, apply 1 to the corresponding multiplexer input.


If the bottom minterm is circled and the top is not circled, apply A to the corresponding multiplexer input.

If the top minterm is circled and the bottom is not circled, apply A' to the corresponding multiplexer input.

Answer: Part (c)


Minterm	A	B	C	F
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	0
7	1	1	1	0

	I_0	I_1	I_2	I_3
A'	0	1	2	3
A	4	5	6	7
	1	A	0	0

 

Built the following function using 4x1 Mux

$$F(A, B, C) = \Sigma(1, 3, 5, 6)$$

 

(a) Multiplexer implementation

Minterm	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

(b) Truth table

	I_0	I_1	I_2	I_3
A'	0	①	2	③
A	4	⑤	⑥	7
	0	1	A	A'

(c) Implementation table

Try it yourself


- a) Implement the below function using a 8x1 Mux.
- b) Implement the below function using a 4x16 decoder and OR gates

$$F(A, B, C, D) = \Sigma(0, 1, 3, 4, 8, 9, 15)$$

Solution

• a)

	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
A'	①	②	3	④	⑤	6	7	
A	⑧	⑨	10	11	12	13	14	⑮
	1	1	0	A'	A'	0	0	A

 

Home-task: Try it yourself

Using 2:1 MUX design

- AND gate
 - OR gate
 - NOT gate
-
- Solution: Try YOUTUBE

Note:


- Both mux and decoder can be used to design combinational circuit.
- Decoder are mostly used to decoding binary information and mux are mostly used to select path between multiple sources and a single destination.

4 variables with 4x1 Mux

Implementation using Multiplexer

$F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$ using 4 x 1 Multiplexer with A, B as input variables and C, D as selection variables


	I_0	I_1	I_2	I_3
$A'B'$	0	1	2	3
$A'B$	4	5	6	7
AB'	8	9	10	11
AB	12	13	14	15
	B	$A \odot B$	AB	$A+B'$

 

A	B	C	D	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

$$F(a,b,c,d) = \sum(0,1,4,5,9,14,15)$$

 Implement the above boolean function using 4:1 MUX(s) and 2:1 MUX(s).




	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
a	0	1	2	3	4	5	6	7
$\bar{a}$	8	9	10	11	12	13	14	15
	$\bar{a}$	1	0	0	$\bar{a}$	$\bar{a}$	a	a

Combining MSI to build
Combinational Design Circuit

Exercise time!

- Design a BCD to Excess 3 code converter using '4x16' decoder and '16x4' encoder

Solution

 

Try it yourself

- Design a full adder using '3x8' decoder and '4x2' encoder

Solution:

